



Ve270 Introduction to Logic Design

Homework 1

Assigned: May 14, 2020

Due: May 21, 2020, 2:00pm.

A pop quiz will be given on the due date.

1. Fill out the blank spaces, assuming unsigned numbers. Show steps to earn partial credits. (8 points)

$$11011101.001_2 = \underline{\hspace{2cm}}_{10} = \underline{\hspace{2cm}}_{16}$$

$$63.89_{10} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_8 = \underline{\hspace{2cm}}_3$$

2. Fill out the blank spaces, assuming 2's complement numbers. (16 points)

$$-71_{10} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_{16}$$

$$71_{10} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_{16}$$

$$10110101101_2 = \underline{\hspace{2cm}}_{10}$$

$$\text{FBA9}_{16} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_{10}$$

3. Perform the following arithmetic operations step by step, assuming 2's complement numbers: (12 points)

$$(6\text{FA}49\text{D} + 73\text{BD})_{16} =$$

$$(10100 - 10101001)_2 =$$

$$(534 - 265)_8 =$$

4. Problem 2.14 (Boolean equation = logic equation) (4 points)

2.14 Evaluate the Boolean equation $F = a \text{ AND } (b \text{ OR } (c \text{ AND } d))$ for the given values of variables a , b , c , and d :

a. $a=1, b=1, c=0, d=1$

b. $a=0, b=0, c=0, d=1$

c. $a=1, b=0, c=0, d=0$

d. $a=1, b=0, c=1, d=1$

5. Problem 2.16 (10 points)

2.16 Show the conduction paths and output value of the AND gate transistor circuit in Figure 2.14 when: (a) $x = 1$ and $y = 0$, (b) $x = 1$ and $y = 1$.

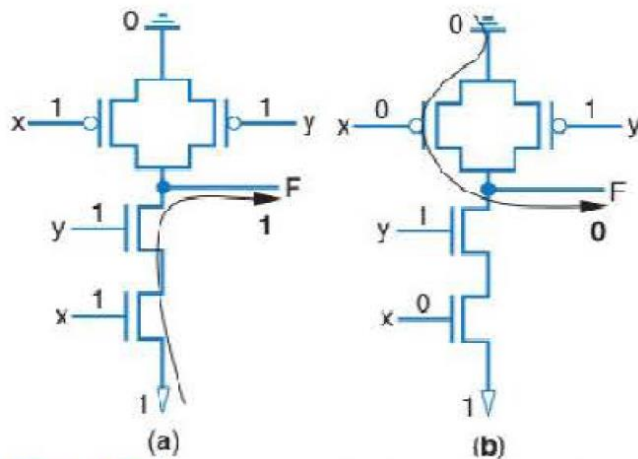


Figure 2.14 AND gate conduction paths: (a) when all inputs are 1, and (b) when any input is 0.

6. Problem 2.19 (10 points)

2.19 Convert each of the following equations directly to gate-level circuits:

a. $F = abc + a'bc$

b. $F = a + bcd' + ae + f'$

c. $F = (a + b) + (c' * (d + e + fg))$

7. Problem 2.20 (10 points)

2.20 Design a system that sounds a buzzer inside a home whenever motion outside is detected at night. Assume a motion sensor has an output M that indicates whether motion is detected ($M=1$ means motion detected) and a light sensor with output L that indicates if light is detected ($L=1$ means light is detected). The buzzer inside the home has a single input B that when 1 sounds the buzzer. Capture the desired system behavior using an equation, and then convert the equation to a circuit using AND, OR, and NOT gates.

8. Problem 2.35 (10 points)

2.35 Convert each of the following Boolean equations to a truth table:


a. $F(a, b, c) = a' + bc'$

b. $F(a, b, c) = (ab)' + ac' + bc$

c. $F(a, b, c) = ab + ac + ab'c' + c'$

d. $F(a, b, c, d) = a'bc + d'$

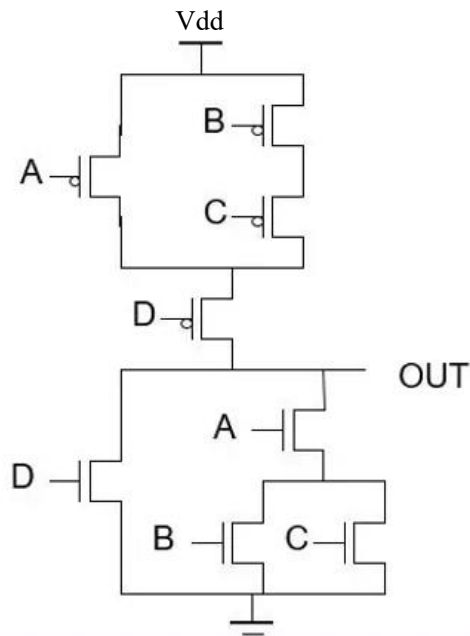9. Build a truth table for the following circuit. (10 points)



10. Given a logic equation $F = a'bc' + b'c + abc$, draw an output waveform for F based on the given input waveforms. (10 points)

