 


Question

10 分

Which of the following timing diagram(s) may be produced with a D Latch?



Sensitive to high level


The correct output of a gated D-Latch sensitive to low level.

Question

15 分

Given a D flip-flop with synchronous active high Clear signal, as well as Clock and D inputs, shown in the following timing diagram, what are the values of output Q (0 or 1) at the moments labelled with the circled numbers? Assume initial value of Q is 1.

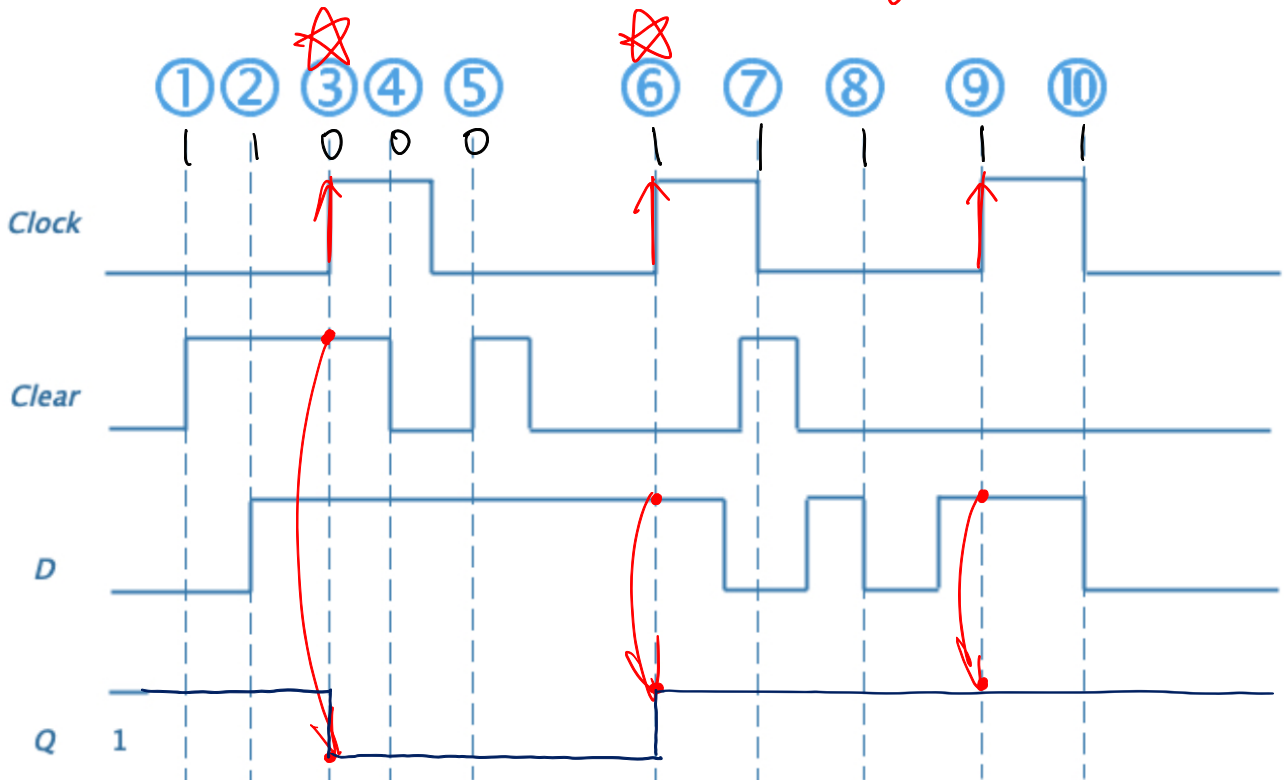Consider ideal situations (No delay at ③, ⑥)




VE 270 Quiz 4 2020.6.11. Candy Candies.
 
### Question

10 分

Given following circuit and timing diagram of its inputs, what are the values of signals A, B, C, and D at the Examine Point of Time?



A small delay before the output of '5'


That is, there is no output value of A at exactly the first rising edge.

So for the second register at the first rising edge it remains to be 'x'

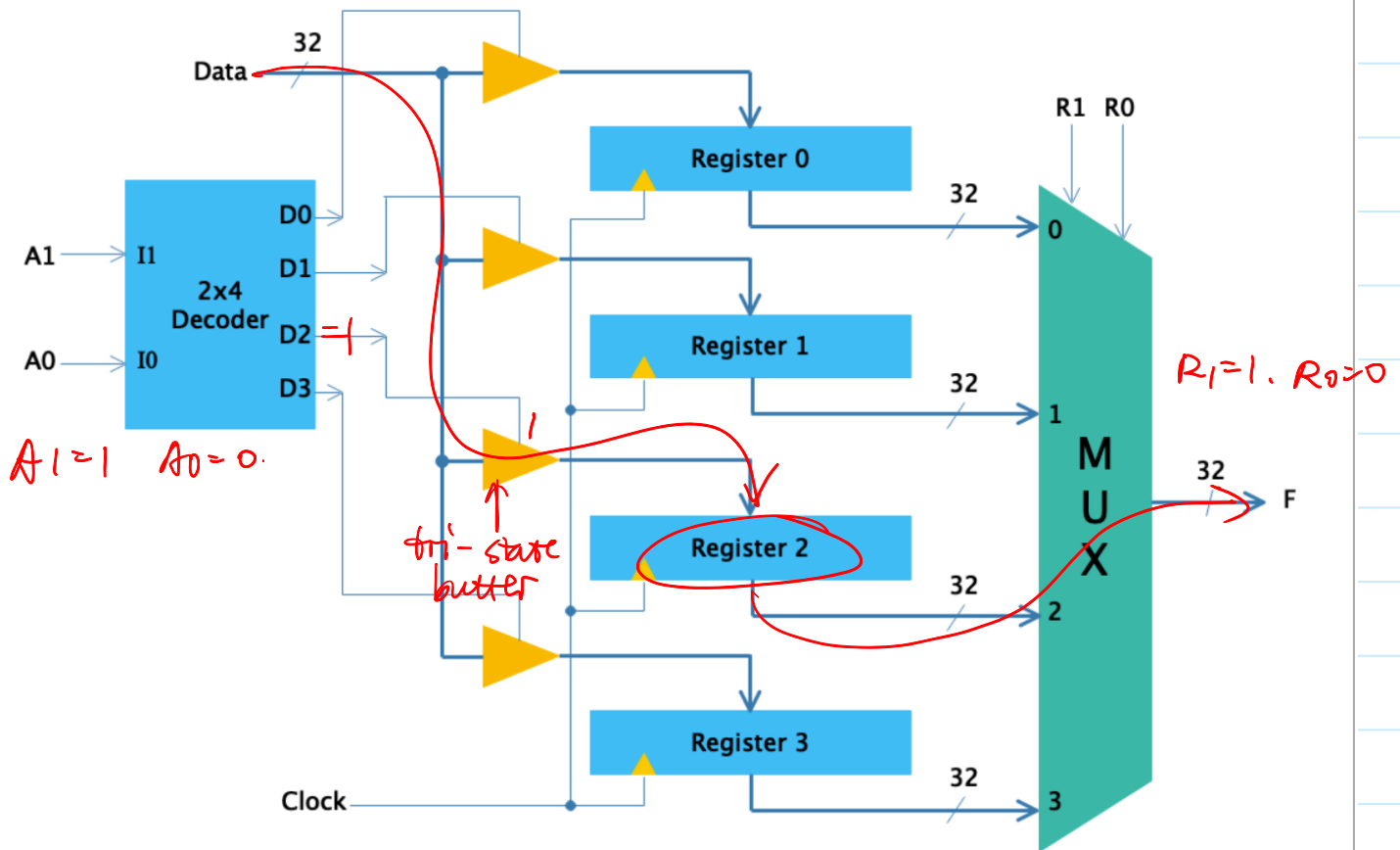Question

15 分

Given the following circuit, describe in text how to store the "Data" input in "Register 2", and then how to put the stored "Data" on the output "F".



① To store the data inputs in "Register 2":

Set  $A1=1, A0=0$  to make the output  $D2$  of the 2x4 Decoder to be 1 which enables the tri-state buffer connected to Register 2. So that Data can pass through this buffer and stored in Register 2 after the rising edge of the clock.

② Put the stored "Data" on the output 'F'.

Set  $R1=1, R0=0$  to let the mux to choose the signal from the port labeled "2" and then output the data (a point).

(a period) pay attention to rising edge / high level. They are different