



**Ve270 Introduction to Logic Design**

**Homework 6**


**Assigned: June 18, 2020**

**Due: July 2, 2020, 2:00pm.**

**A pop quiz will be given on the due date.**

1. Problem 4.2 (10 points)

 - 4.2 Trace the behavior of an 8-bit parallel load register with 8-bit input  $I$ , 8-bit output  $Q$ , load control input  $ld$ , and synchronous clear input  $clr$  by completing the timing diagram in Figure 4.96.



2. Problem 4.3, using components to draw schematic (20 points)

- 4.3 Design a 4-bit register with 2 control inputs  $s1$  and  $s0$ , 4 data inputs  $I3, I2, I1$  and  $I0$ , and 4 data outputs  $Q3, Q2, Q1$  and  $Q0$ . When  $s1s0=00$ , the register maintains its value. When  $s1s0=01$ , the register loads  $I3..I0$ . When  $s1s0=10$ , the register clears itself to 0000. When  $s1s0=11$ , the register complements itself, so for example 0000 would become 1111, and 1010 would become 0101. (*Component design problem*).

3. Problem 4.45. Draw schematic. (20 Points).

- 4.45 Design a circuit whose 16-bit output is nine times its 16-bit input  $D$  representing an unsigned binary number. Ignore overflow issues. (*Component use problem*.)

4. Problem 4.57. Draw schematic (a), (b). (20 points)


- 4.57 Design a circuit that outputs a 1 every 99 clock cycles:

- Using an up-counter with a synchronous clear control input, and using extra logic,
- Using a down-counter with parallel load, and using extra logic.

5. Problem 4.59. Draw schematic (10 Points)

4.59 Create a clock divider that converts a 14 MHz clock into a 1 MHz clock. Use a down-counter with parallel load. Clearly indicate the width of the down counter and the counter's load value. (Component use problem.)

 6. Model a Universal Shift Register (shown below) with Verilog. Simulate your design. (20 Points)



Inputs		Action
Sh (Shift)	L (Load)	
0	0	no change
0	1	load
1	X	Shift Right