

# **VE270 Recitation Class**

**2020.7.8**

Yiqing Zhao



# Outline

- Registers
  - A. Register with Load Signal
  - B. Shift Register&Rotate Register
  - C. Universal Shift Register
  - D. Register Examples
- Shifters
  - A. Bigger Shifter
- Finite State Machine
  - A. FSM (Controller) Design

# Registers
  
## General Description


- Registers: Sets of Flip-Flops, can store data



# Registers
 
## General Description



```
module Reg_N_bits (Q, Din, clock);  
    parameter size = 4;  
    input clock;  
    input [size-1:0] Din;  
    output reg [size-1:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q <= Din;  
    end  
endmodule
```



# Registers
 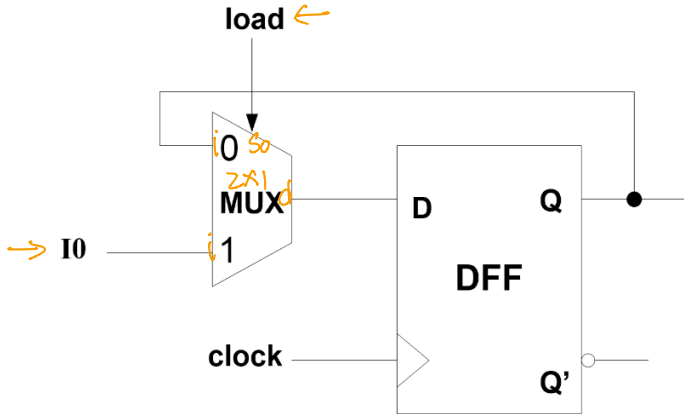
## Register with Load Signal


- When  $\text{load} = 1$ , we can load the value of the current input



# Registers
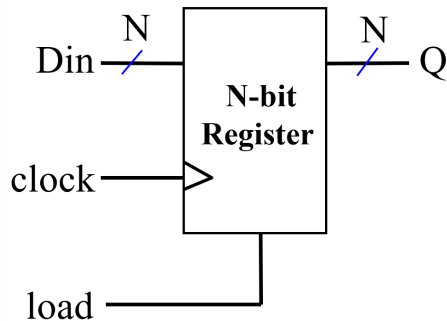
## Register with Load Signal


```
module Reg_N_bits (Q, Din, clock, load);  
    parameter size = 4;  
    input clock, load;  
    input [size-1:0] Din;  
    output reg [size-1:0] Q;  
  
    always @ (posedge clock)  
    begin  
        if (load) Q <= Din;  
    end  
endmodule
```



# Registers

 
## Shift Registers & Rotate Registers

- Shift Registers: Connect Q output of one flip-flop to the D input of the next flip-flop
- Rotate Registers: The same as shift registers, but connect Q output of last flip-flop to the D input of the first flip-flop



Suppose IN = 1, Init = 0011:

0011->1001->1100->1110->1111

 

Suppose Init = 0011:

0011->1001->1100->0110->0011

# Registers

## Shift Registers & Rotate Registers

```
module Shift_Reg (Q, Dout, Din, clock);  
    input clock, Din;  
    output Dout;  
    output reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3] <= Din;  
    end  
  
    assign Dout = Q[0];  
endmodule
```



# Registers

## Shift Registers & Rotate Registers

```
module Barral_Shift_Reg (Q, clock);  
    input clock;  
    output reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3] <= Q[0];  
    end  
endmodule
```




# Registers

## ★ Universal Shift Register

- Multi-functional Shift Register: Shift Right, Load, Hold, ...

$$\text{Load} = D_3 D_2 D_1 D_0$$

Labels

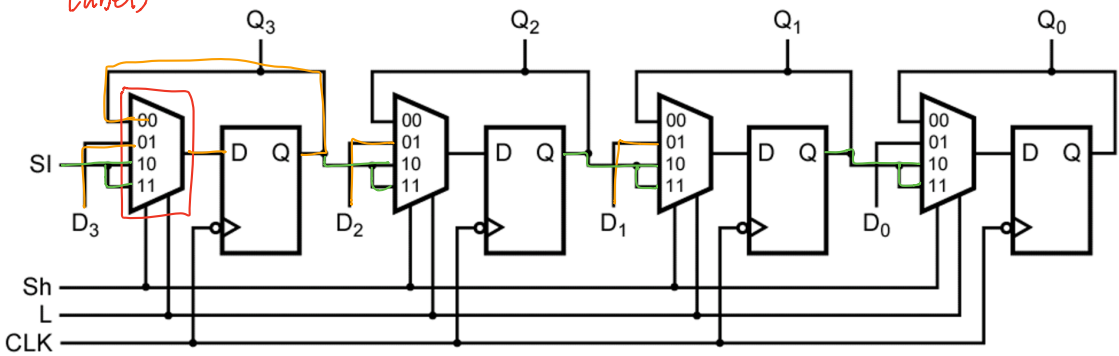

Sh(Shift)	L(Load)	Action
0	0	Hold
0	1	Load
1	X	Shift Right

# Registers

## Universal Shift Register


- Design a register with the following control signals:

Sh(Shift)	L(Load)	Action
0	0	Hold
0	1	Load
1	0	Shift Left
1	1	3*Content

$$\underline{Q_3 Q_2 Q_1 Q_0} \times 2 + Q_3 Q_2 Q_1 Q_0$$

$$Q_3 Q_2 Q_1 Q_0 0$$


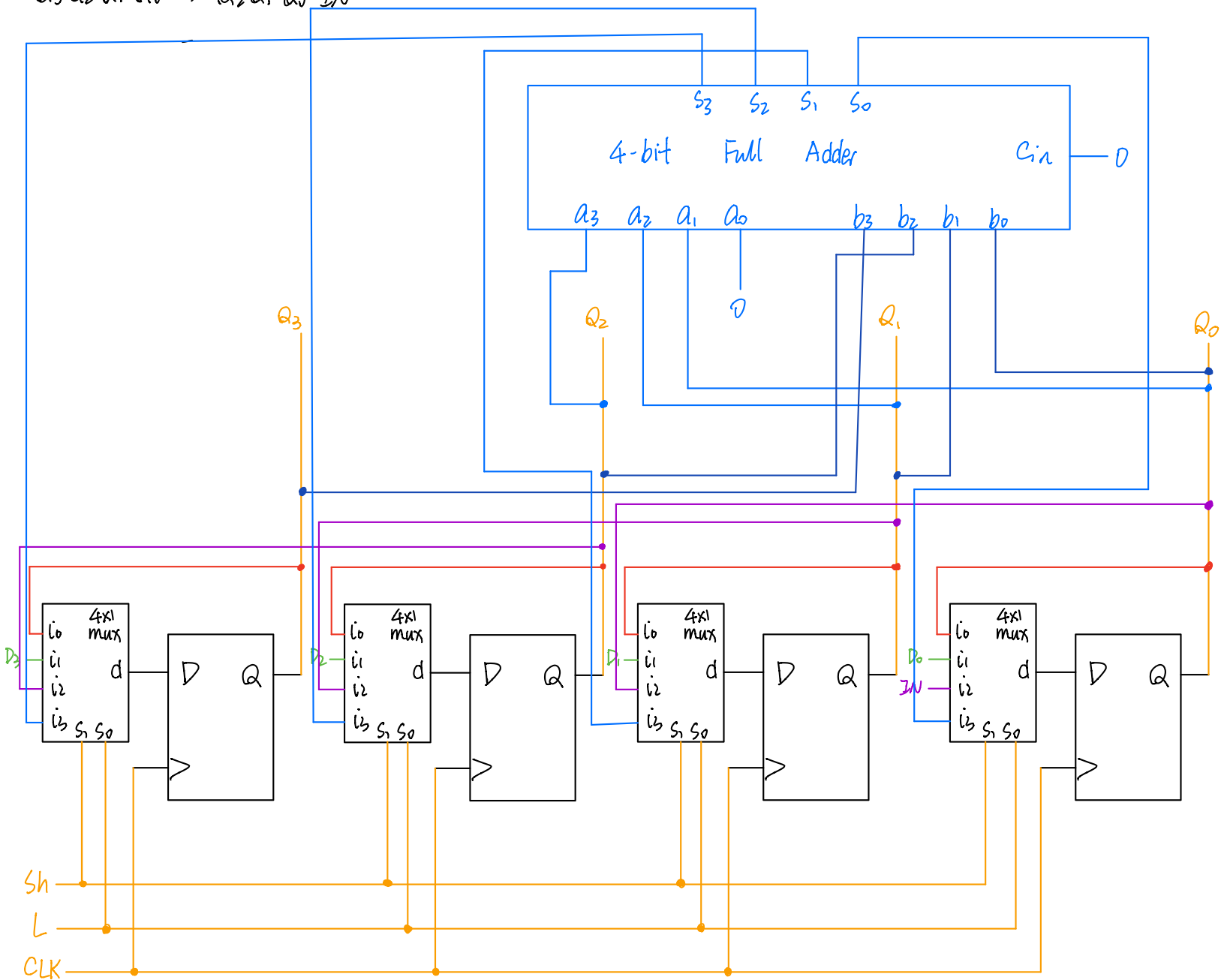
$$Q_3 Q_2 Q_1 Q_0 \Rightarrow Q_2 Q_1 Q_0 IN$$



# Registers

## Register Examples


- Above-Mirror Display

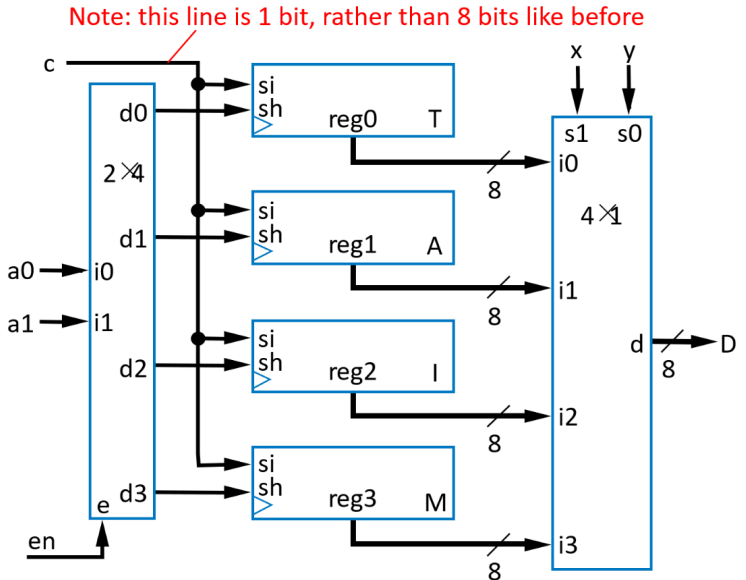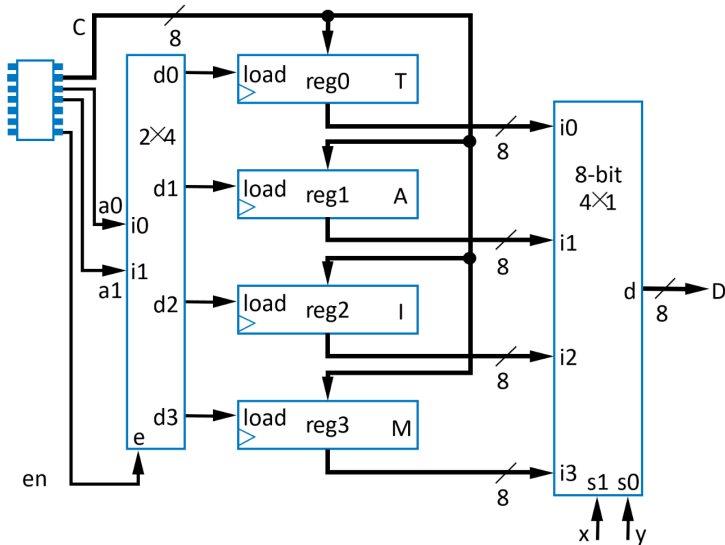

# Registers

## Register Examples



- Register File

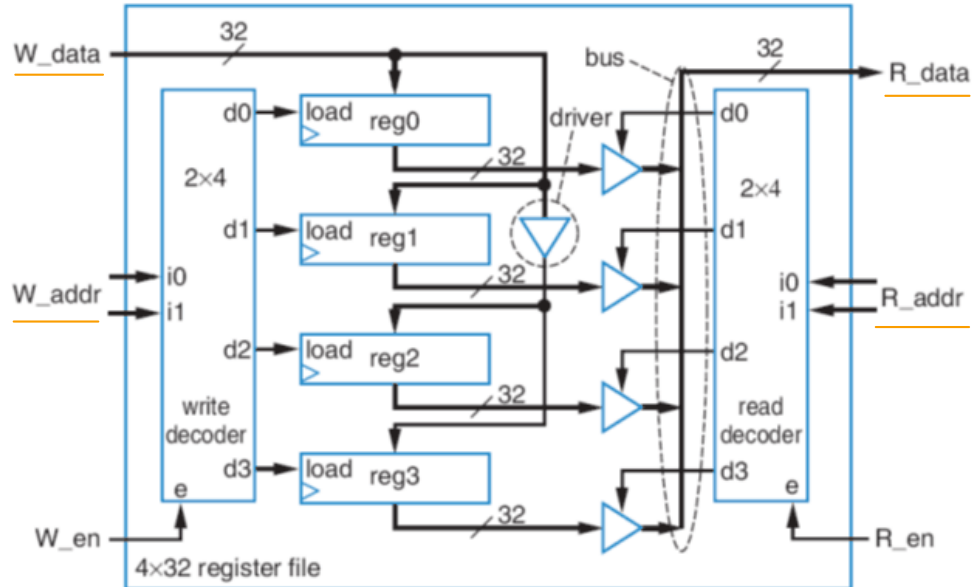

# Shifters
  
## General Description

- Shifters are not Shift Registers: Shifters use MUX, and change value immediately
- $X \gg 1$  equals  $X/2$
- $X \ll 1$  equals  $X * 2$




# Shifters

## Bigger Shifter

- A shifter that can shift by any amount - By using multiple shifters
- To shift I by N,  $4x+2y+z = N$ , where  $x, y, z = 0$  or  $1$ .

Q: xyz=??? to  
shift I by 5?

 




# Finite State Machine
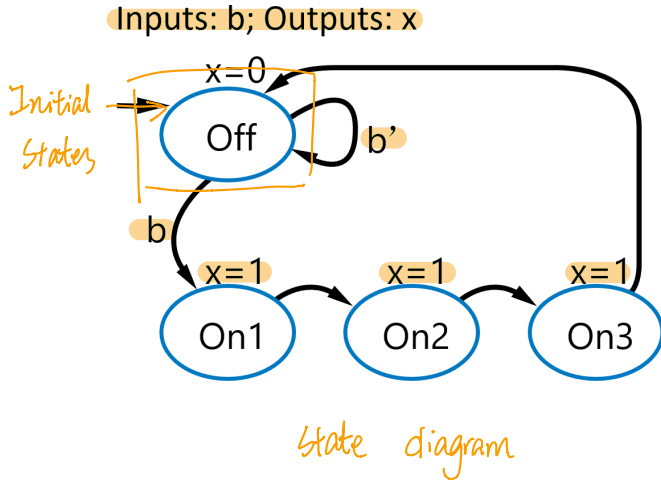
## General Description

- Finite State Machine (FSM) has states, inputs, outputs, initial state, transitions.
- State Diagram & State Table:



State table.

		Inputs			Outputs			
Present State		s1	s0	b	x	n1	n0	next state
00	Off	0	0	0	0	0	0	
		0	0	1	0	0	1	
01	On1	0	1	0	1	1	0	
		0	1	1	1	1	0	
10	On2	1	0	0	1	1	1	
		1	0	1	1	1	1	
11	On3	1	1	0	1	0	0	
		1	1	1	1	0	0	

# Finite State Machine

## FSM (Controller) Design

- Five steps:
  1. Capture the FSM
  2. Create the architecture
  3. Encode the states
  4. Create the state table
  5. Implement the combinational logic

# Finite State Machine


## FSM (Controller) Design

- One day, Engineering students are rushing to Long Bin Building from their dorms on Xuanhuai Avenue. They are busy reading about FSMs in their favorite textbook and aren't looking where they are going.
- At the same time, Math students are rushing the 5th Canteen to get their favorite Pan Fried dumplings on Longpo Road. They are solving differential equations in their minds and aren't looking where they are going either.
- Then, a serious injury occurs at the intersection of the two roads. A student, Bit, decides to solve this problem by using FSM.

# Finite State Machine
 
## FSM (Controller) Design


- Bit uses two traffic sensors,  $T_A$  and  $T_B$ , on Xuanhuai Ave. and Longpo Road, respectively.
  - Sensors show 0: students present
  - Sensors show 1: students not present
- Bit uses two traffic lights,  $L_A$  and  $L_B$ , to control traffic. The traffic lights has three mode.  
(Green: 00, Yellow: 01, Red: 10)



# Finite State Machine
 
## FSM (Controller) Design


- The FSM controller updates on the rising edge of the clock signal:
  - At beginning, the lights are green on Xuanhuai Ave. and red on Longpo Road.
  - If traffic appears on Xuanhuai Ave., the lights do not change. When there is no longer traffic on Xuanhuai Ave., the light on Xuanhuai Ave. becomes yellow for a clock cycle before it turns red and Longpo road's light turns green.
  - Similarly, the Longpo road's light remains green as long as traffic is present, then turns yellow and eventually red.



# Finite State Machine
 
## FSM (Controller) Design

- Step 1: Capture the FSM
  - Among all transitions leaving a state, only one condition should be true.
  - Among all transitions leaving a state, one condition must be true.
  - All conditions must be considered when leaving a state.





$L_A, L_B = 2 \text{ bits}$   
 $T_A, T_B = 1 \text{ bit}$

# Finite State Machine

## FSM (Controller) Design

- Step 2: Create the architecture

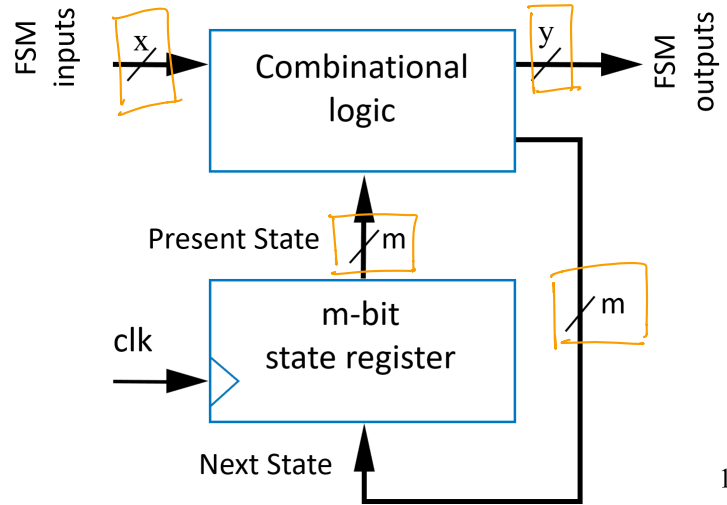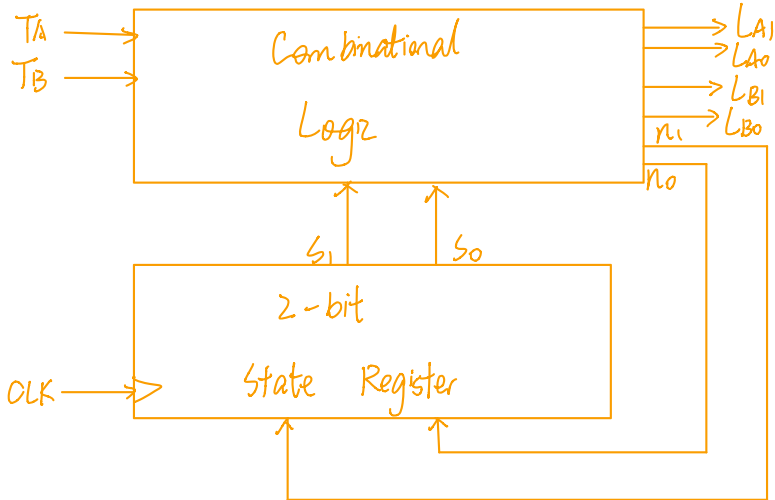

# Finite State Machine

## FSM (Controller) Design

- Step 3: Encode the states

$$s_0 = 00$$

$$s_1 = 01$$

$$s_2 = 10$$


$$s_3 = 11$$



# Finite State Machine

## FSM (Controller) Design

- Step 4: Create the state table

 

Present State		Input		Next State		Output			
S <sub>i</sub>	S <sub>o</sub>	TA	TB	N <sub>i</sub>	N <sub>o</sub>	LA <sub>i</sub>	LA <sub>o</sub>	LB <sub>i</sub>	LB <sub>o</sub>
0	0	0	X	0	1	0	0	1	0
0	0	1	X	0	0	0	0	1	0
0	1	X	X	1	0	0	1	1	0
1	0	X	0	1	1	1	0	0	0
1	0	X	1	1	0	1	0	0	0
1	1	X	X	0	0	1	0	0	1

# Finite State Machine

## FSM (Controller) Design

- Step 5: Implement the combinational logic

$$N_1 = S_1'S_0 + \underline{S_1S_0'T_B'} + S_1S_0'T_B = S_1'S_0 + S_1S_0' = S_1 \oplus S_0$$


$$N_0 = S_1'S_0'T_A' + S_1S_0'T_B'$$

$$L_{A1} = S_1S_0' + S_1S_0 = S_1$$

$$L_{A0} = S_1'S_0$$

$$L_{B1} = S_1'S_0' + S_1'S_0 = S_1'$$

$$L_{B0} = S_1S_0$$

 

**Any Questions?**