
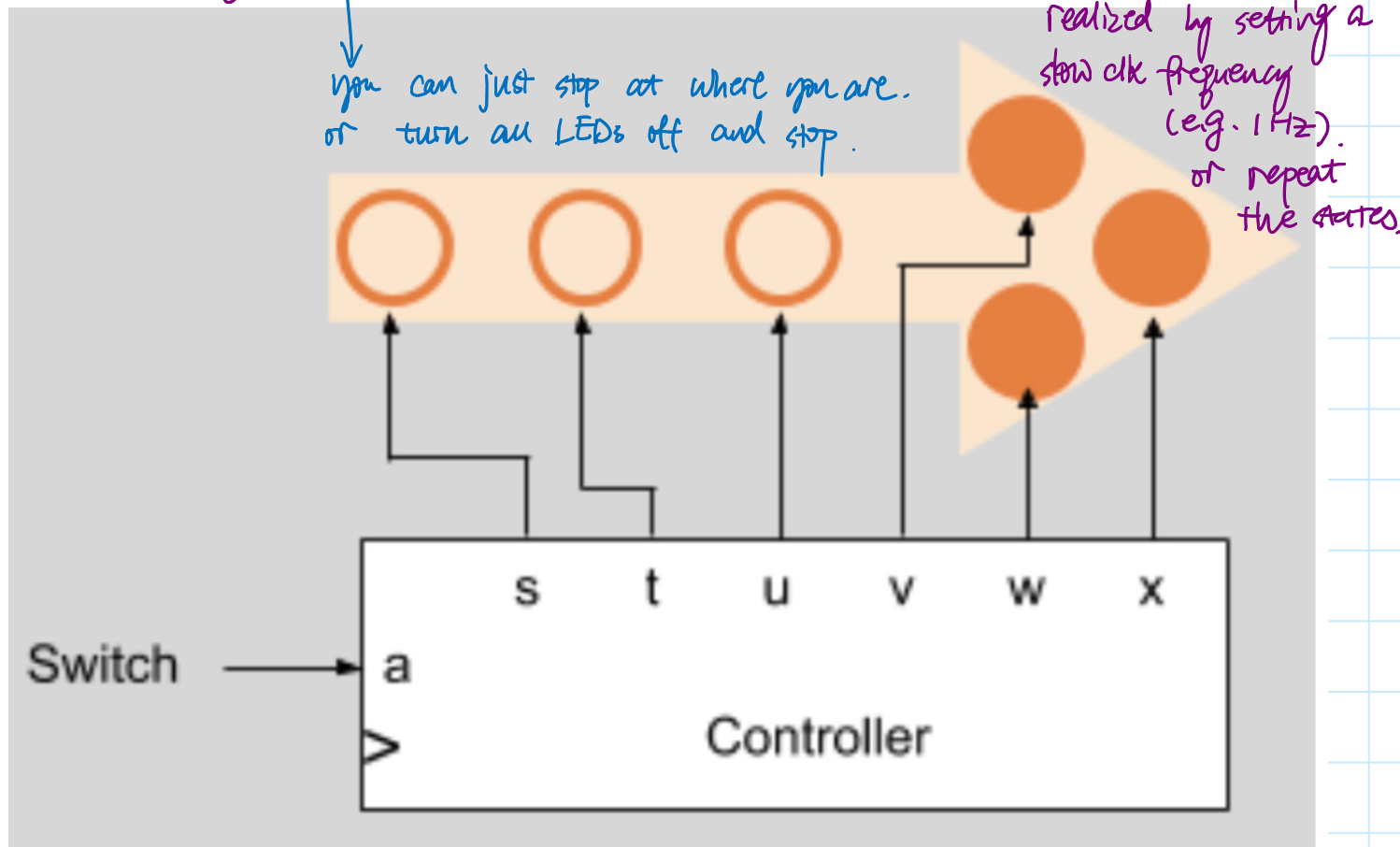


A highway construction sign illuminates LEDs to tell drivers to move over, as illustrated below. The behavior can be captured as an FSM to generate the necessary output sequence: LEDs connected to outputs s, t, u will be turned on sequentially, before the 3 LEDs in the triangle area are all turned on at the same time. Then all of them will be turned off and repeat. Input a = 1 activates the sequence or it will stop the illumination, controlled by a switch on the sign. Make sure the LEDs are on for sufficient amount of time (your decision).

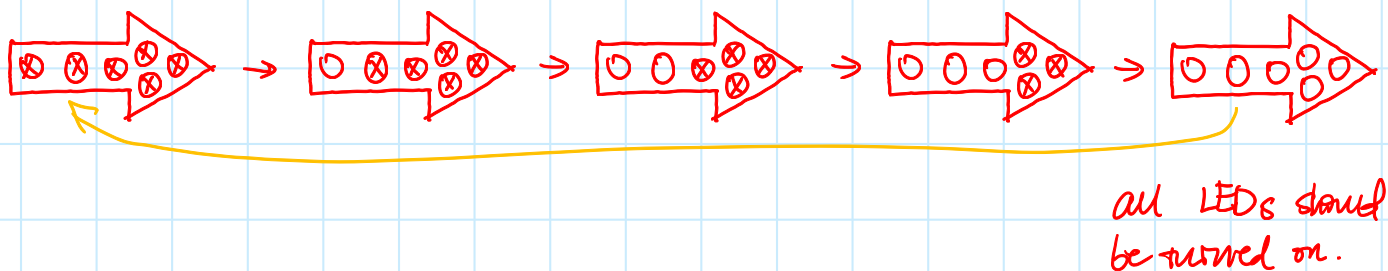


- capture the FSM behavior in a state diagram. (30 points)
- Create the state table with the states encoded. (10 points)
- Draw standard architecture of the FSM. (10 points) (Don't have to show details of the combinational circuit)



VE 270 Quiz 7 2020.7.16 Candy-Candies

Method 1.

(a) Input: a Output: s, t, u, v, w, x clk freq.: 1 Hz.

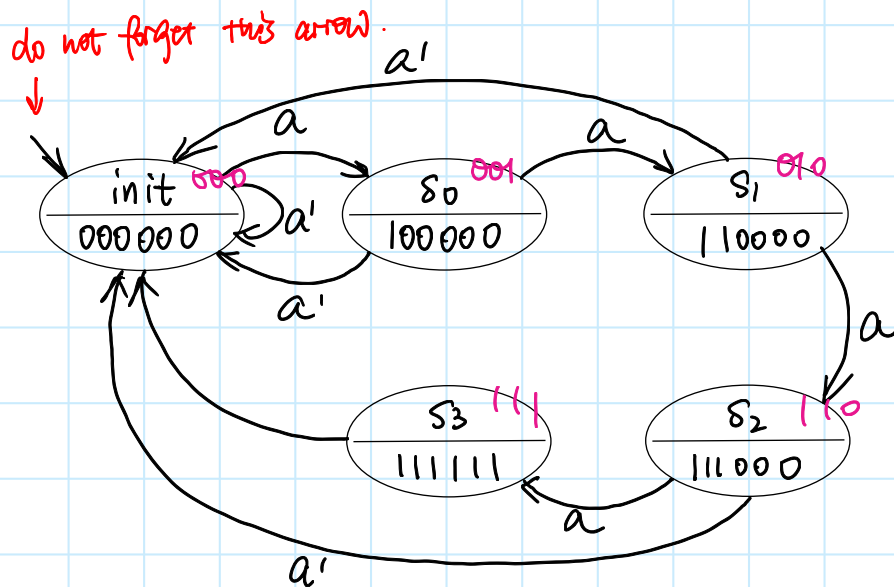

VE 270

Quiz 7

2020. 7. 16

Candy- Candies

(b)


s_2	s_1	s_0	a	n_2	n_1	n_0	s	τ	u	v	w	x
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0	0
0	0	1	1	0	1	0	1	0	0	0	0	0
0	1	0	0	0	0	0	1	1	0	0	0	0
0	1	0	1	0	1	1	1	1	0	0	0	0
0	1	1	0	0	0	0	1	1	1	0	0	0
0	1	1	1	1	0	0	1	1	1	0	0	0
1	0	0	0	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	1	1	1	1	1	1
1	0	1	0	x	x	x	x	x	x	x	x	x
1	0	1	1	x	x	x	x	x	x	x	x	x
1	1	0	0	x	x	x	x	x	x	x	x	x
1	1	0	1	x	x	x	x	x	x	x	x	x
1	1	1	0	x	x	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x	x	x

The output of the present state.


VE 270 Quiz 7 2020. 7. 16

Candy - Candies

(9)

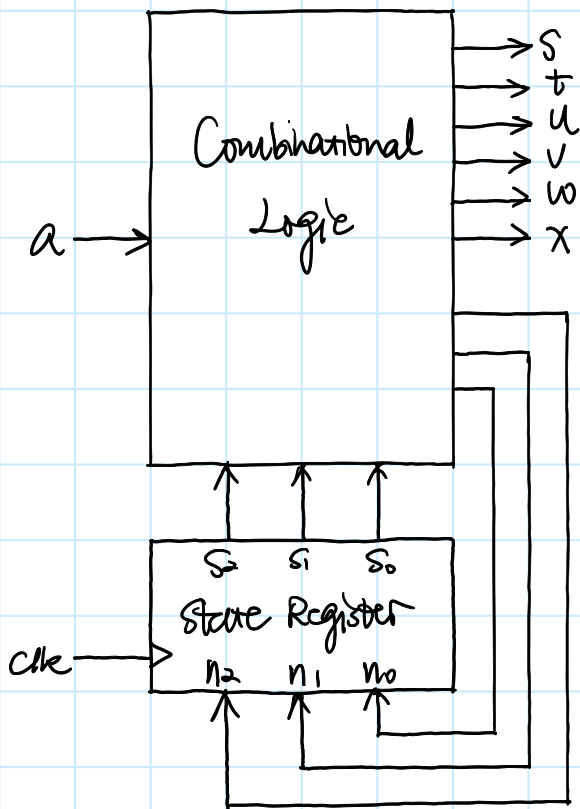

Method 2

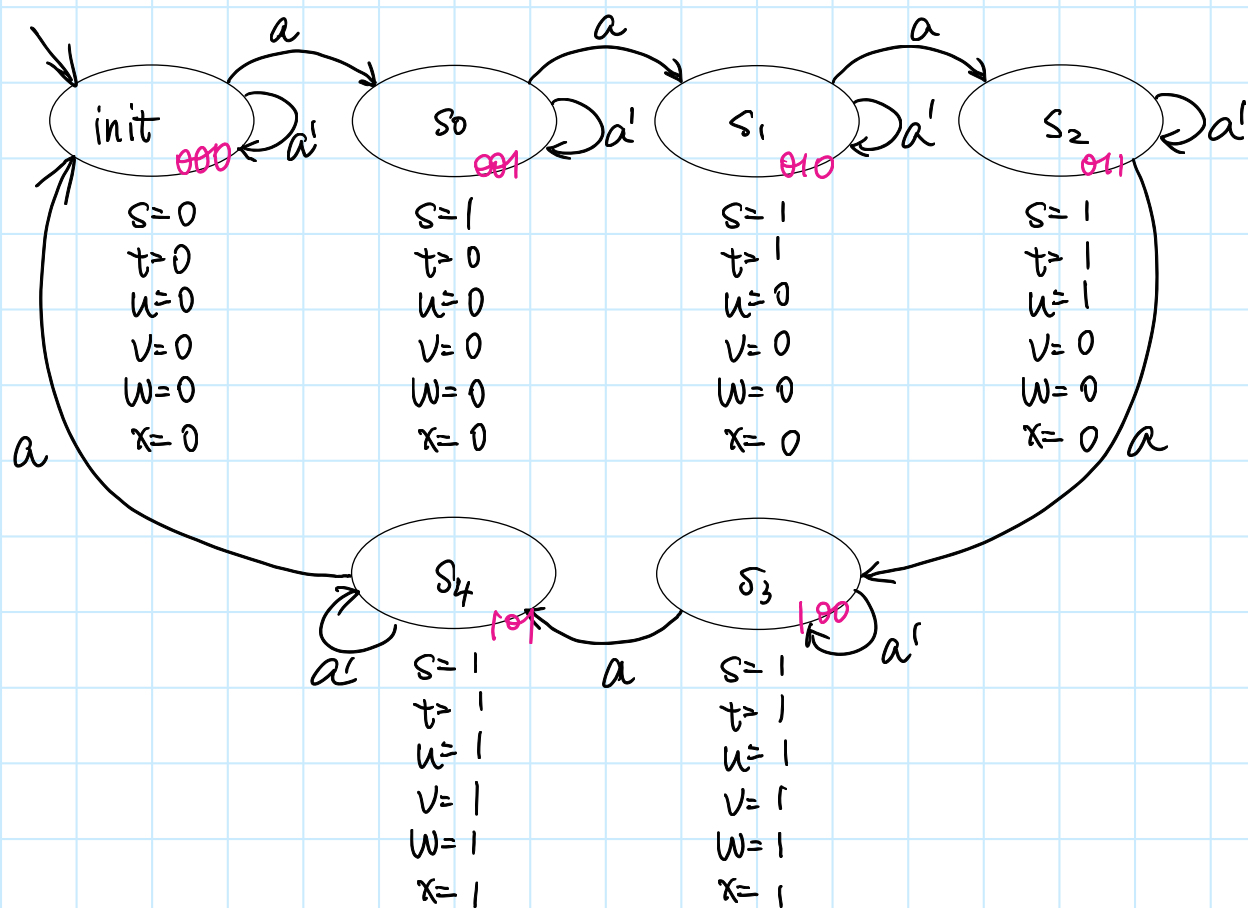(a) Input: a Output: s, t, u, v, w, x 

You can just repeat this state or repeat all the states.

Candy - Candies

[illegible]

VE 270 Quiz 7 2020. 7. 16

Candy - Candies

(9)

