

Ve270 Introduction to Logic Design

Homework 9


Assigned: July 21, 2020

Due: July 28, 2020, 2:00pm.


A pop quiz will be given on July 30.

- Design a circuit called **Receiver** that receives two single bit signals, **Valid** and **Data_in**, from another device called **Transmitter**. The **Valid** signal sent from the **Transmitter** will be a 1-clock cycle pulse. After the **Receiver** receives the **Valid** pulse, it will start receiving 8 bits through port **Data_in**, bit by bit. After the 8 bits of data is received, they should be copied into an 8-bit register called **RxReg**. (25 points)

 HLSM Input: Valid, Data_in (1 bit)
Local register: i (3 bit), data (8 bit), RxReg (8 bit)




Datapath

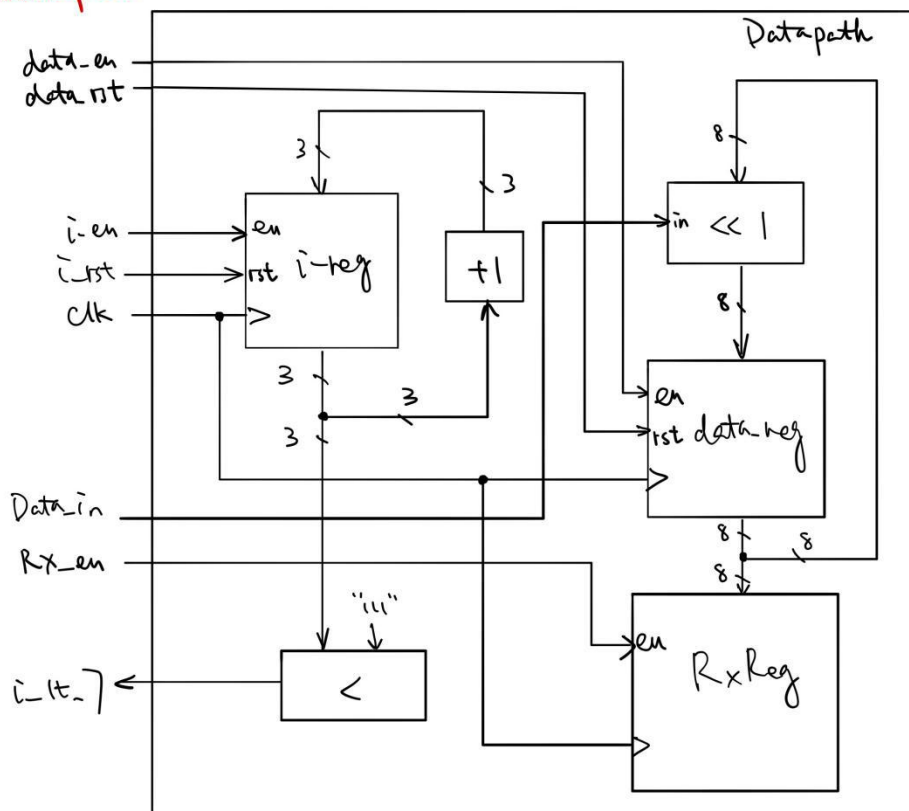


FSM.

Input: Valid, i_lt_7 (bit)

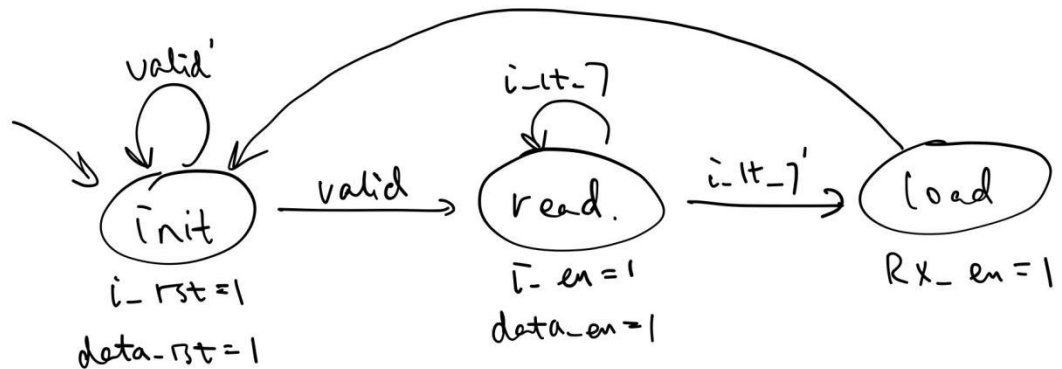Output: i_en , i_rst , $data_en$, $data_rst$, Rx_en (bit).



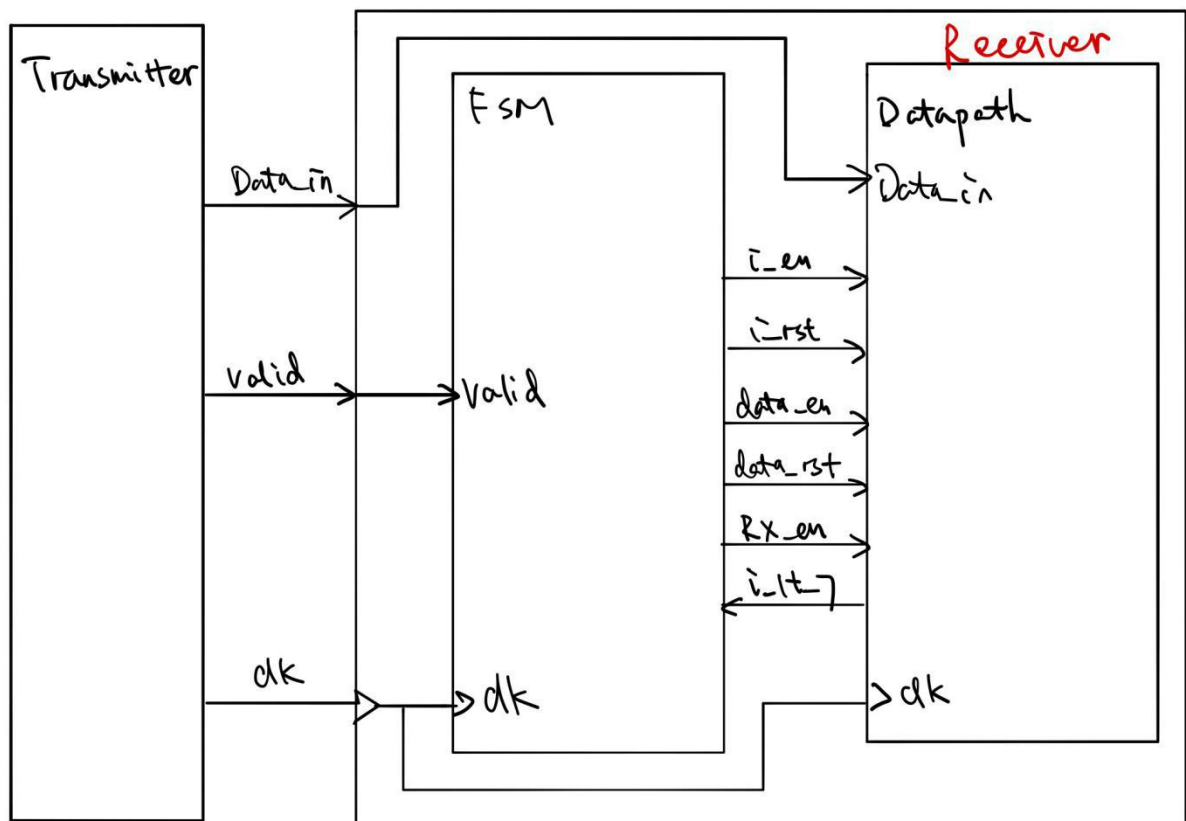Implement the circuit of FSM. (omitted here).




2. Problem 5.19 (25 points)

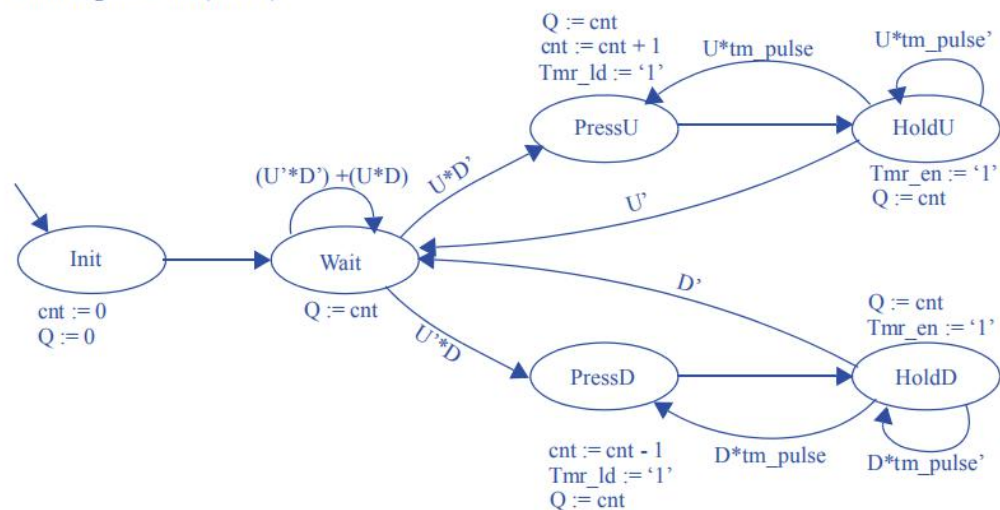
5.19 Using a timer, design a system with single-bit inputs U and D corresponding to two buttons, and a 16-bit output Q which is initially 0. Pressing the button for U causes Q to increment, while D causes a decrement; pressing both buttons causes Q to stay the same. If a single button is held down, Q should then continue to increment or decrement at a rate of once per second as long as the button is held. Assume the buttons are already debounced. Assume Q simply rolls over if its upper or lower value is reached.

Step 1 - Capture a high-level state machine


Inputs: U , D , tm_pulse (bit)
Outputs: Q (16 bits), Tmr_ld , Tmr_en (bit)
Local Registers: cnt (16 bits)



Step 2A - Create a datapath

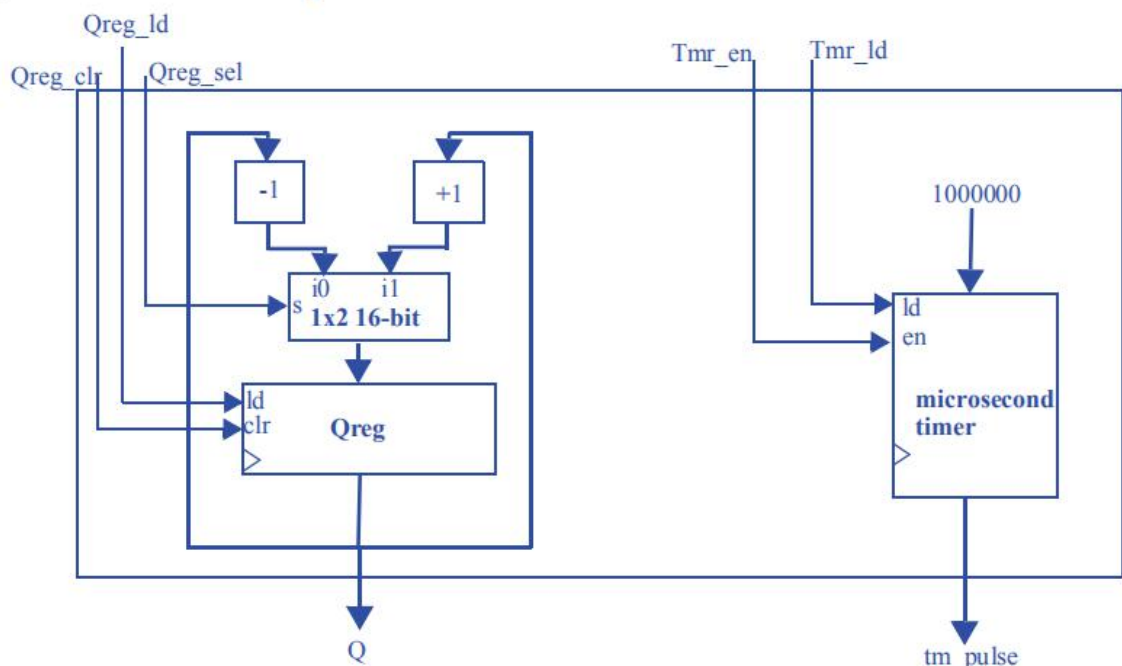

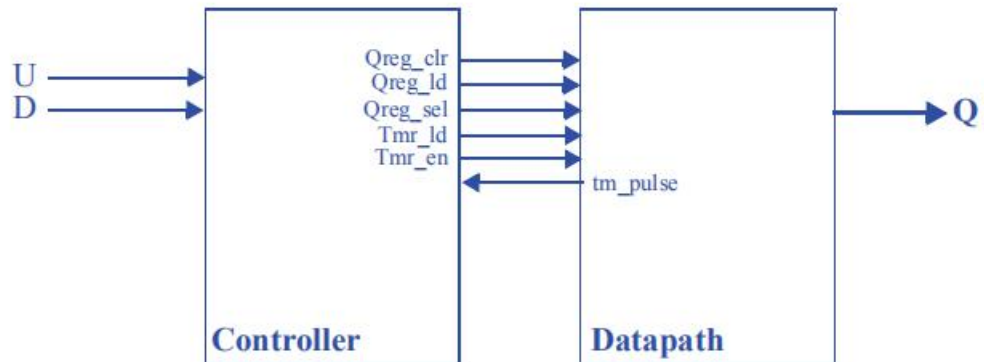
Step 2B - Connect the datapath to a controller



Step 2C - Derive the controller's FSM

Inputs: U, D, tm_pulse

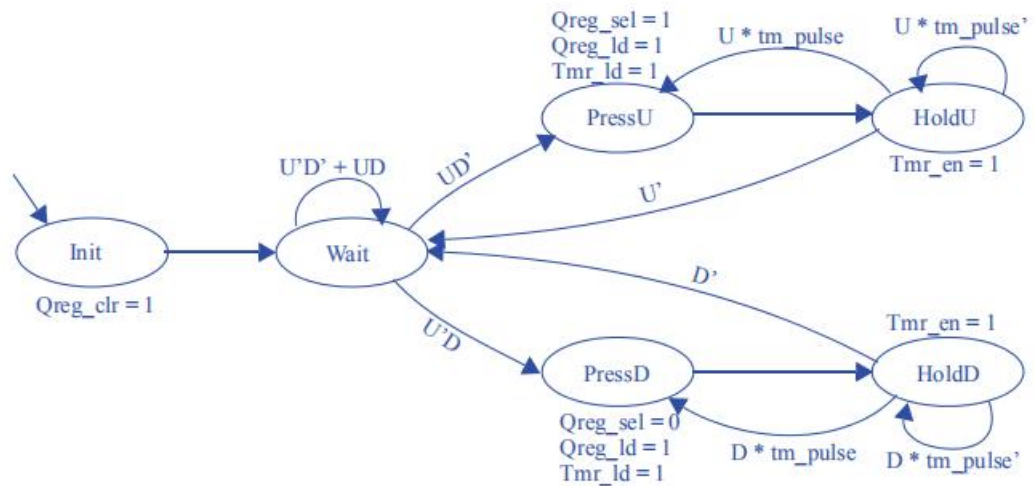Outputs: Qreg_clr, Qreg_ld, Qregsel, Tmr_ld, Tmr_en



3. Problem 5.27 (15 points)

5.27 Convert the following C-like code, which calculates the greatest common divisor (GCD) of the two 8-bit numbers a and b , into a high-level state machine.

Inputs: byte a , byte b , bit go

Outputs: byte gcd , bit $done$


GCD:

```
while(1) {
    while(!go);
    done = 0;
    while ( a != b ) {
        if( a > b ) {
            a = a - b;
        }
        else {
            b = b - a;
        }
    }
    gcd = a;
    done = 1;
}
```

Inputs: go (bit), a , b (8 bits)

Outputs: $done$ (bit), gcd (8 bits)

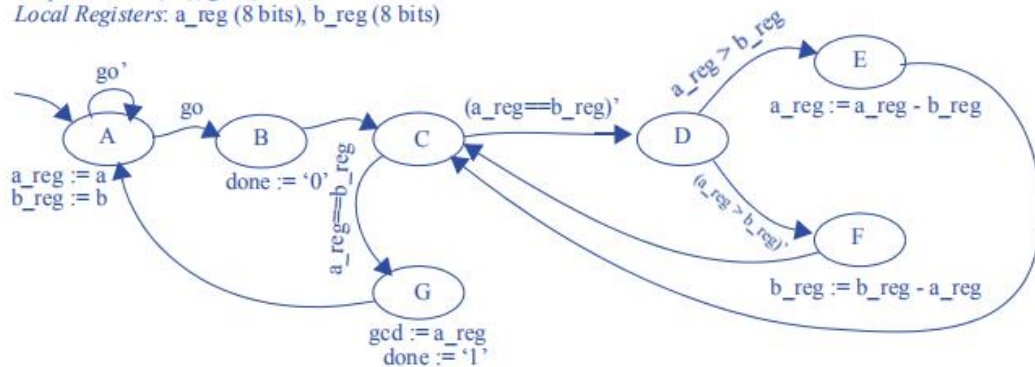Local Registers: a_reg (8 bits), b_reg (8 bits)




4. Problem 5.28 (15 points)

5.28 Use the RTL design process to convert the high-level state machine you created in Exercise 5.27 to a controller and a datapath. Design the datapath to structure, but design the controller to the point of an FSM only.


Step 1 - Capture a high-level state machine

The high-level state machine was developed in Exercise 5.27.

Step 2 - Create a datapath

 


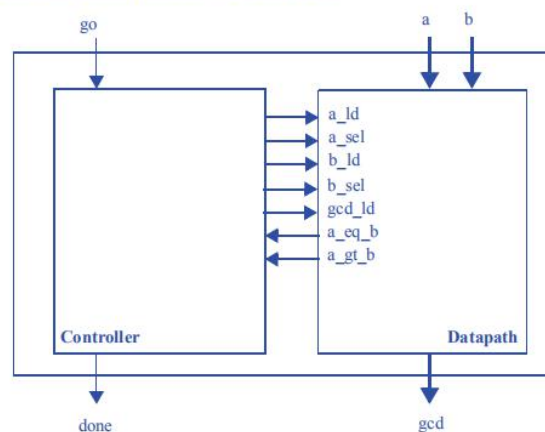Step 3 - Connect the datapath to a controller




Step 4 - Derive the controller's FSM

 
Inputs: `go`, `done`, `a_gt_b`, `a_eq_b` (bit)
Outputs: `done`, `a_ld`, `a_sel`, `b_ld`, `b_sel`, `gcd_ld` (bit)



5. Problem 6.27 (10 points)

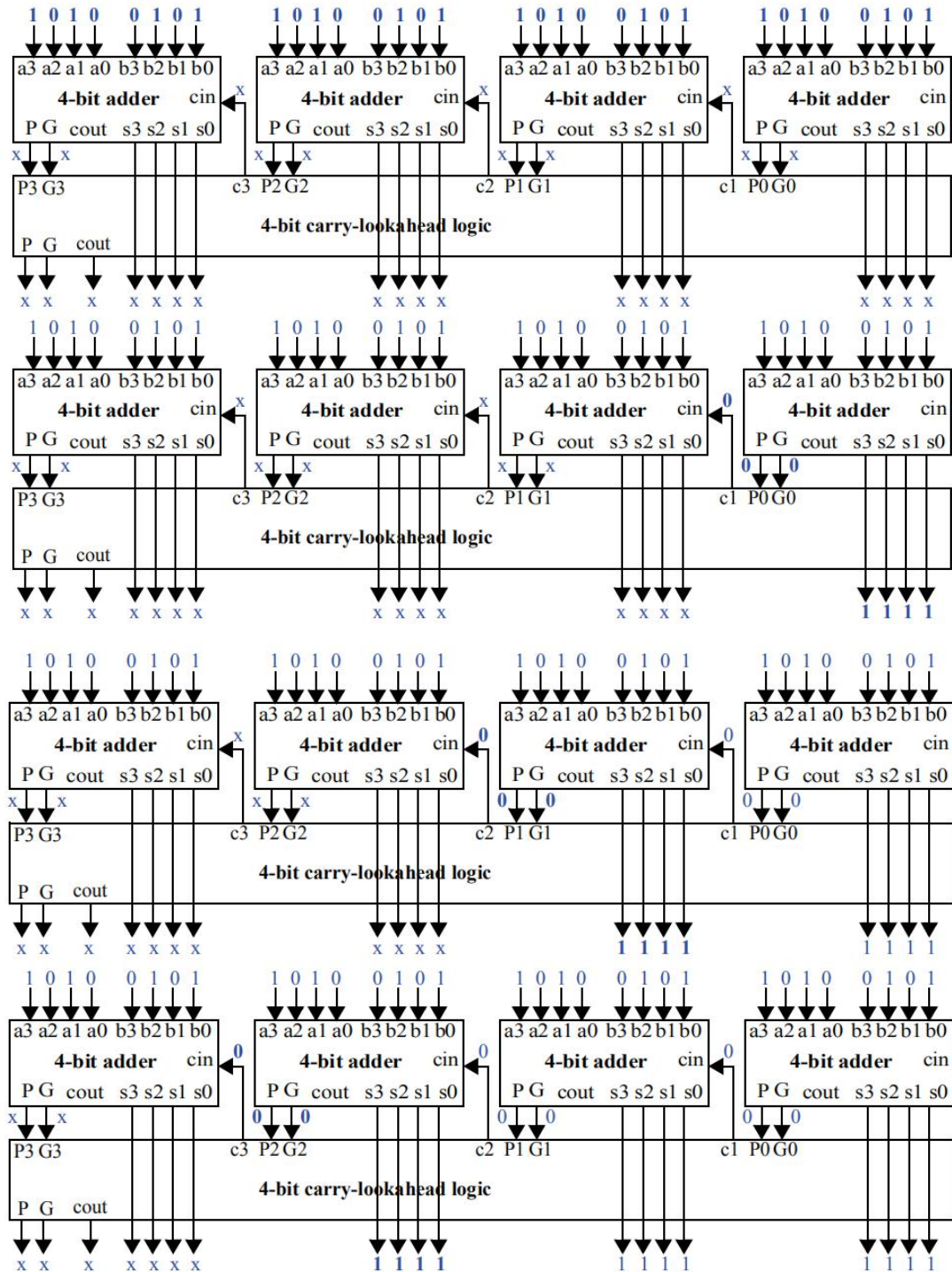6.27) Trace the execution of the 16-bit carry-lookahead adder built from 4-bit adders as shown in Figure 6.60 when $a = 43690$ and $b = 21845$. Do not trace internal behavior of the individual 4-bit carry-lookahead adders..



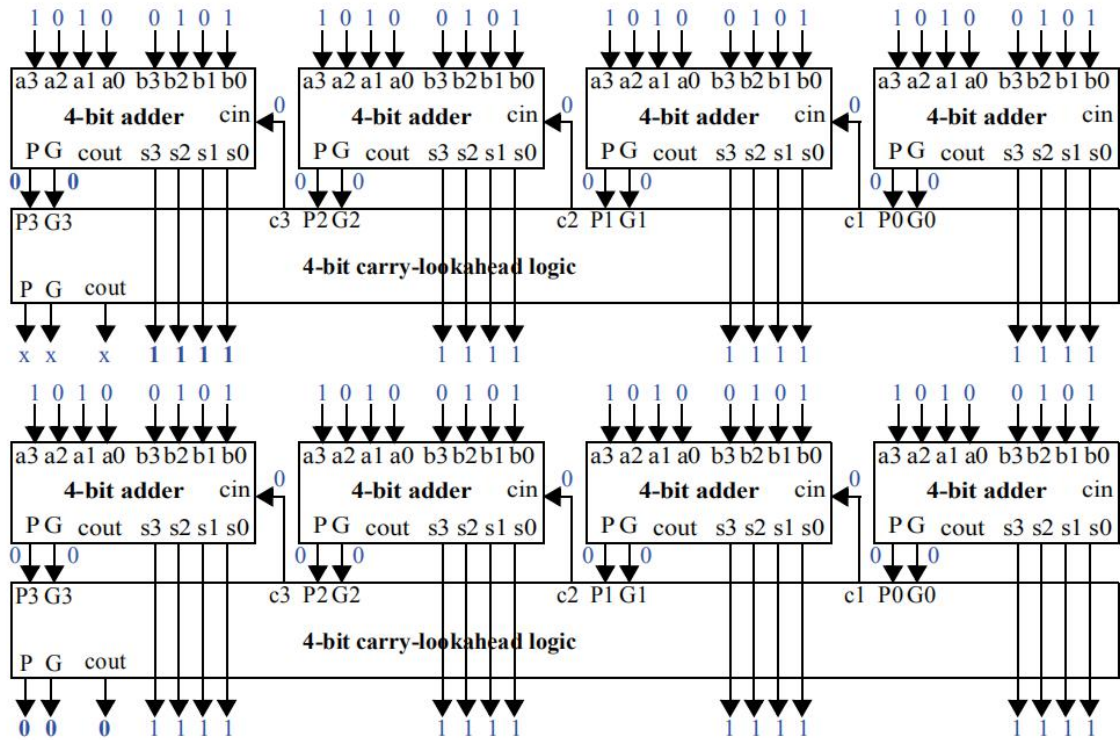

6. Following circuit is a carry-ripple style incrementor. Redesign the circuit as a carry-lookahead structure using the same Half Adders (HA). (10 points)

