

VE270 Recitation Class

2020.7.8

Yiqing Zhao



Outline

- Registers
 - A. Register with Load Signal
 - B. Shift Register&Rotate Register
 - C. Universal Shift Register
 - D. Register Examples
- Shifters
 - A. Bigger Shifter
- Finite State Machine
 - A. FSM (Controller) Design

Registers

General Description

 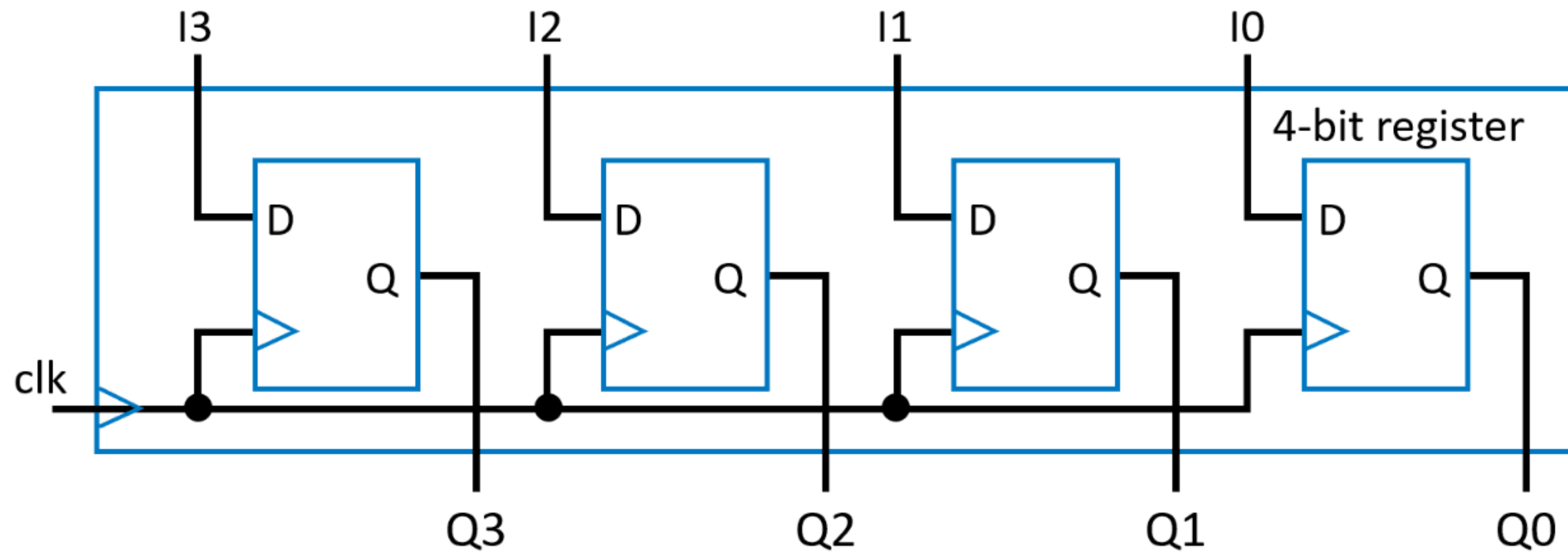
- Registers: Sets of Flip-Flops, can store data



Registers

General Description


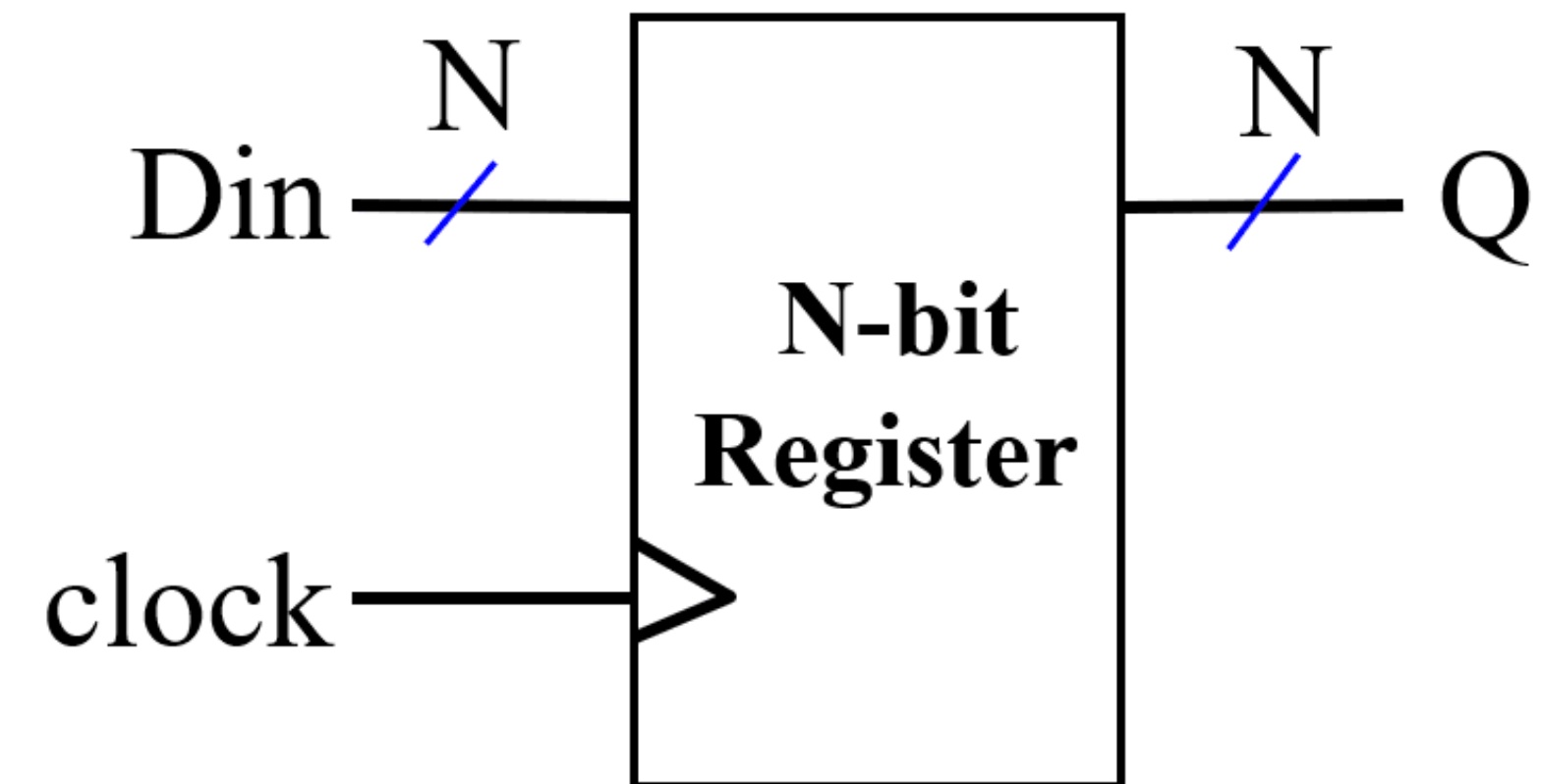
```
module Reg_N_bits (Q, Din, clock);  
    parameter size = 4;  
    input clock;  
    input [size-1:0] Din;  
    output reg [size-1:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q <= Din;  
    end  
endmodule
```



Registers

Register with Load Signal

 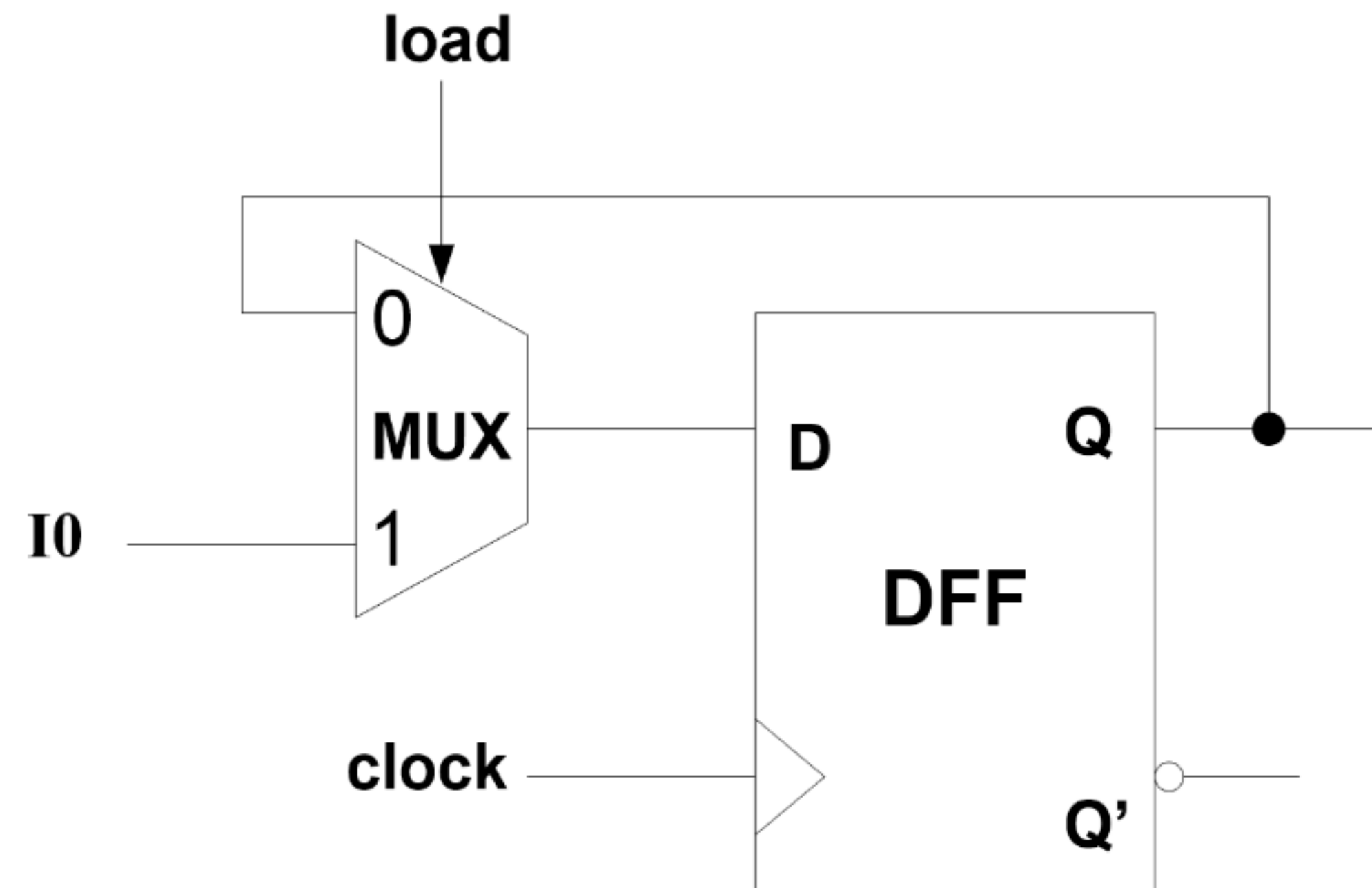
- When $\text{load} = 1$, we can load the value of the current input



Registers

Register with Load Signal

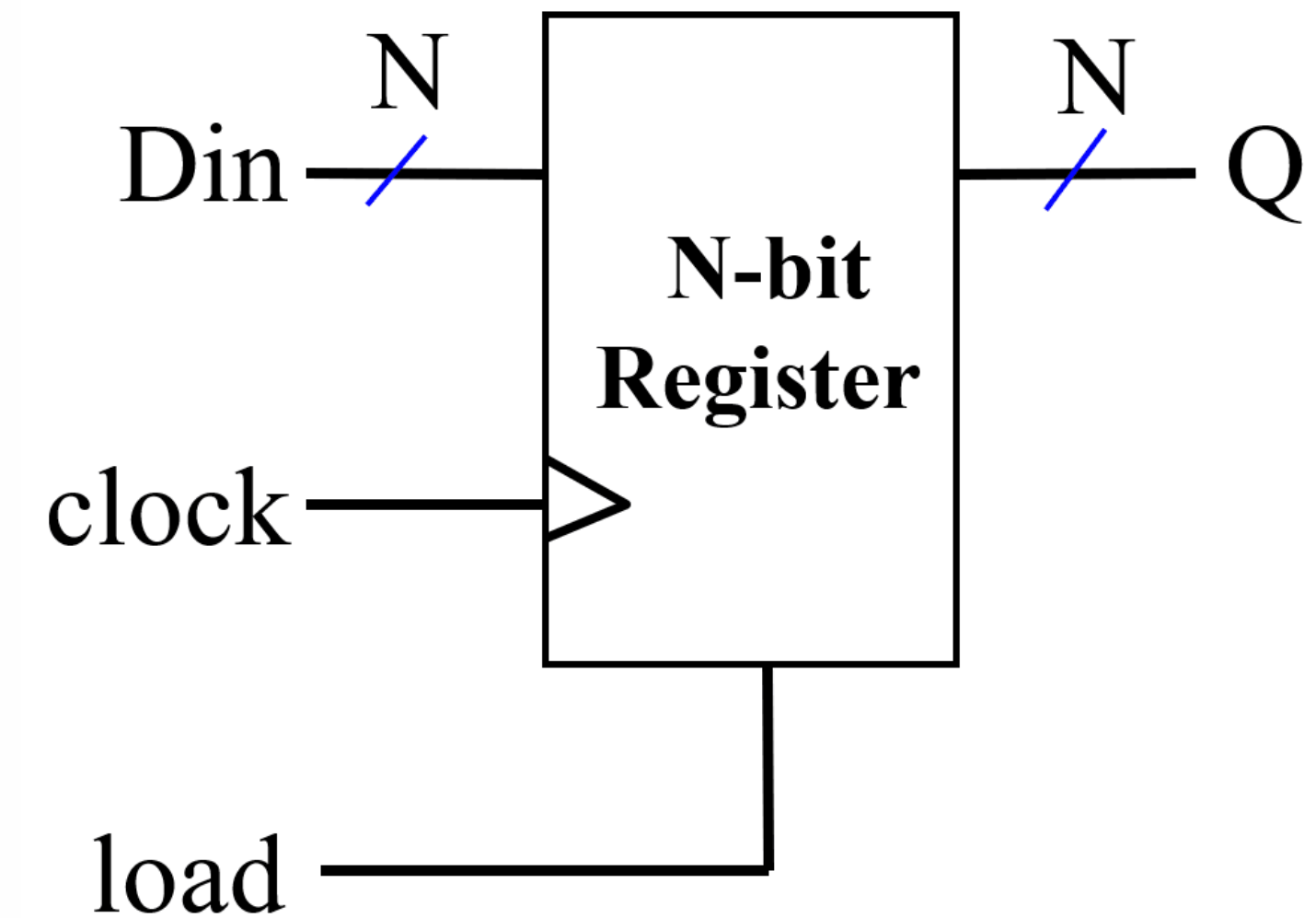
```
module Reg_N_bits (Q, Din, clock, load);  
    parameter size = 4;  
    input clock, load;  
    input [size-1:0] Din;  
    output reg [size-1:0] Q;  
  
    always @ (posedge clock)  
    begin  
        if (load) Q <= Din;  
    end  
endmodule
```




Registers

Shift Registers & Rotate Registers

 - Shift Registers: Connect Q output of one flip-flop to the D input of the next flip-flop
- Rotate Registers: The same as shift registers, but connect Q output of last flip-flop to the D input of the first flip-flop



 Suppose $IN = 1$, $Init = 0011$:
 $0011 \rightarrow 1001 \rightarrow 1100 \rightarrow 1110 \rightarrow 1111$



Suppose $Init = 0011$:
 $0011 \rightarrow 1001 \rightarrow 1100 \rightarrow 0110 \rightarrow 0011$

Registers

Shift Registers & Rotate Registers

```
module Shift_Reg (Q, Dout, Din, clock);  
    input clock, Din;  
    output Dout;  
    output reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3] <= Din;  
    end  
  
    assign Dout = Q[0];  
endmodule
```


Registers


Shift Registers & Rotate Registers

```
module Barral_Shift_Reg (Q, clock);  
    input clock;  
    output reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3] <= Q[0];  
    end  
endmodule
```

Registers

Universal Shift Register

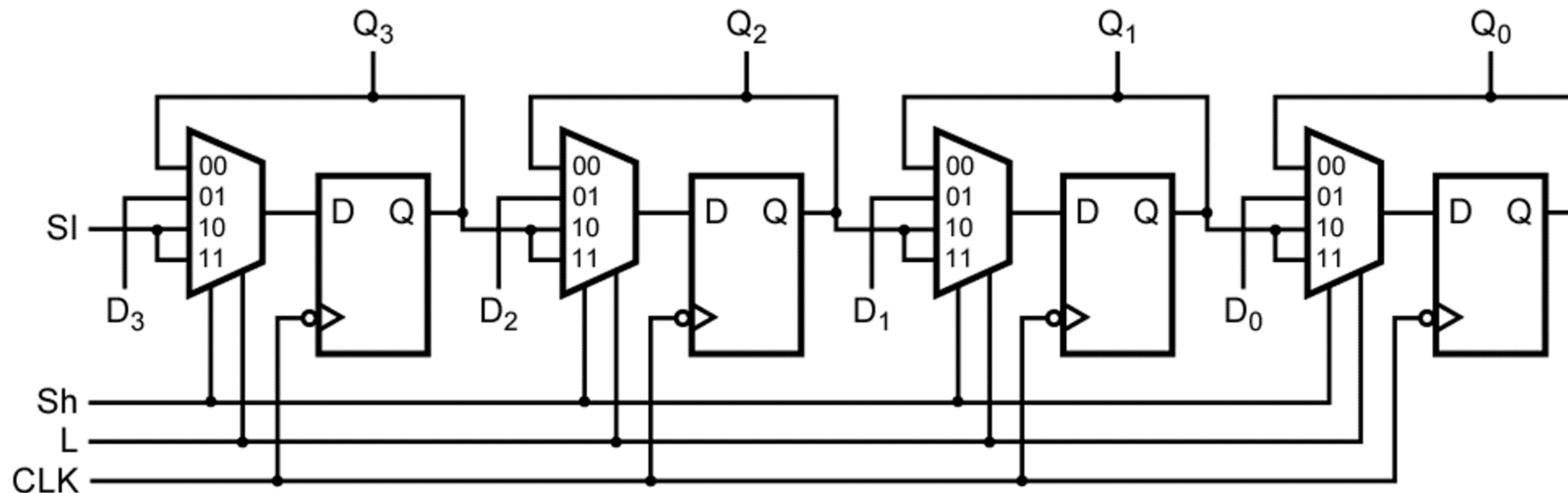- Multi-functional Shift Register: Shift Right, Load, Hold, ...



Sh(Shift)	L(Load)	Action
0	0	Hold
0	1	Load
1	X	Shift Right

Registers

Universal Shift Register



- Design a register with the following control signals:

Sh(Shift)	L(Load)	Action
0	0	Hold
0	1	Load
1	0	Shift Left
1	1	3*Content

Registers

Register Examples


- Above-Mirror Display

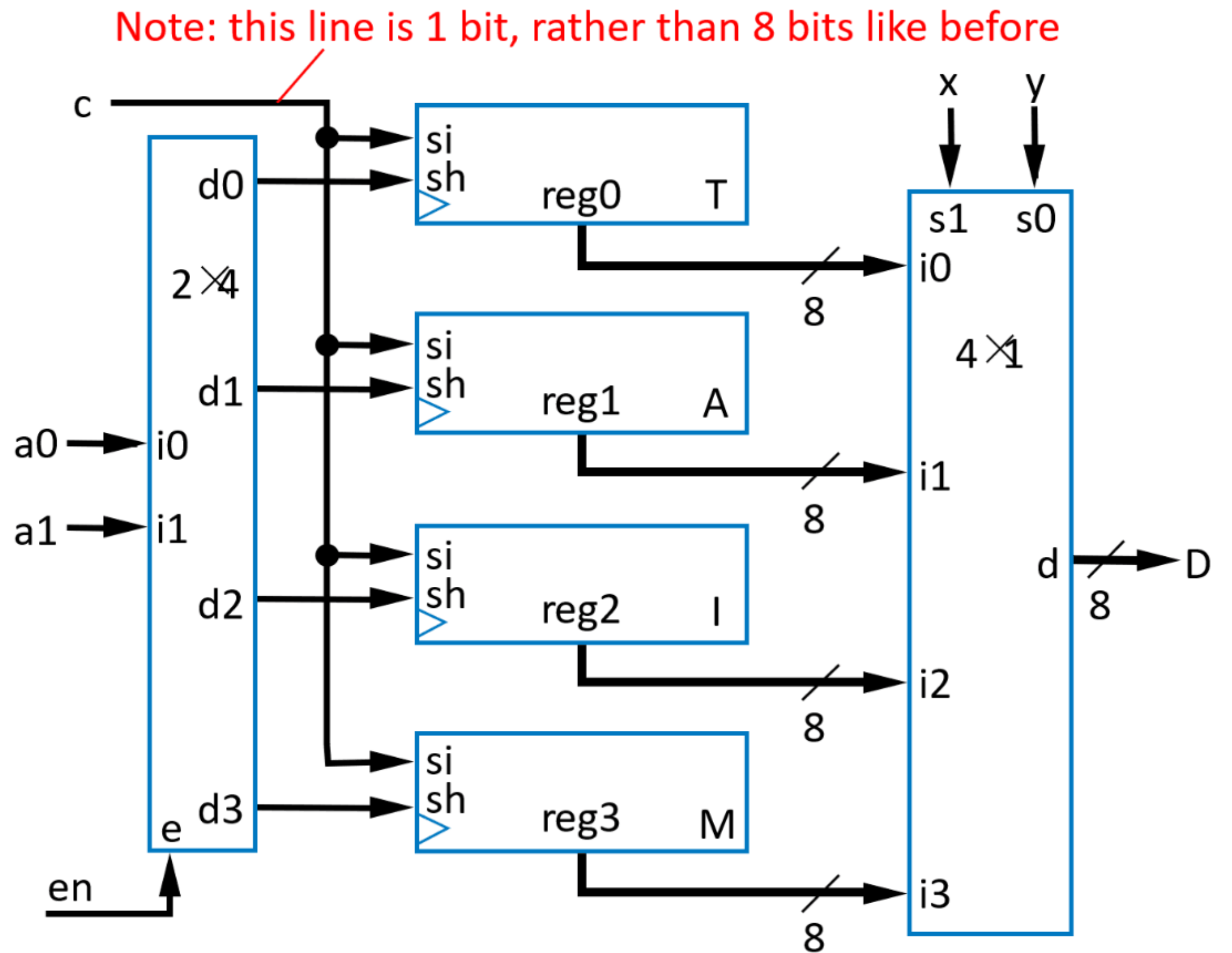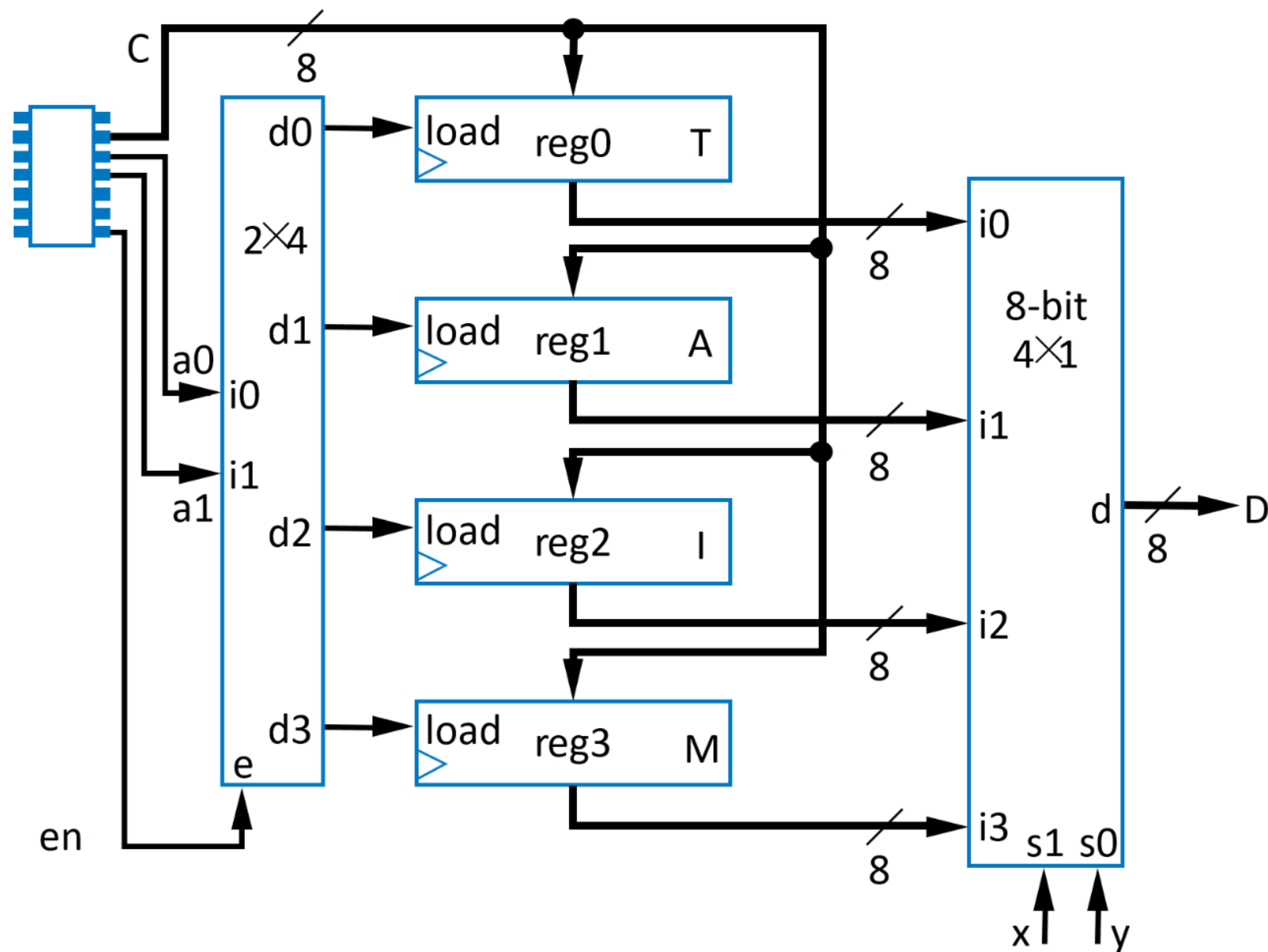

Registers

Register Examples



- Register File

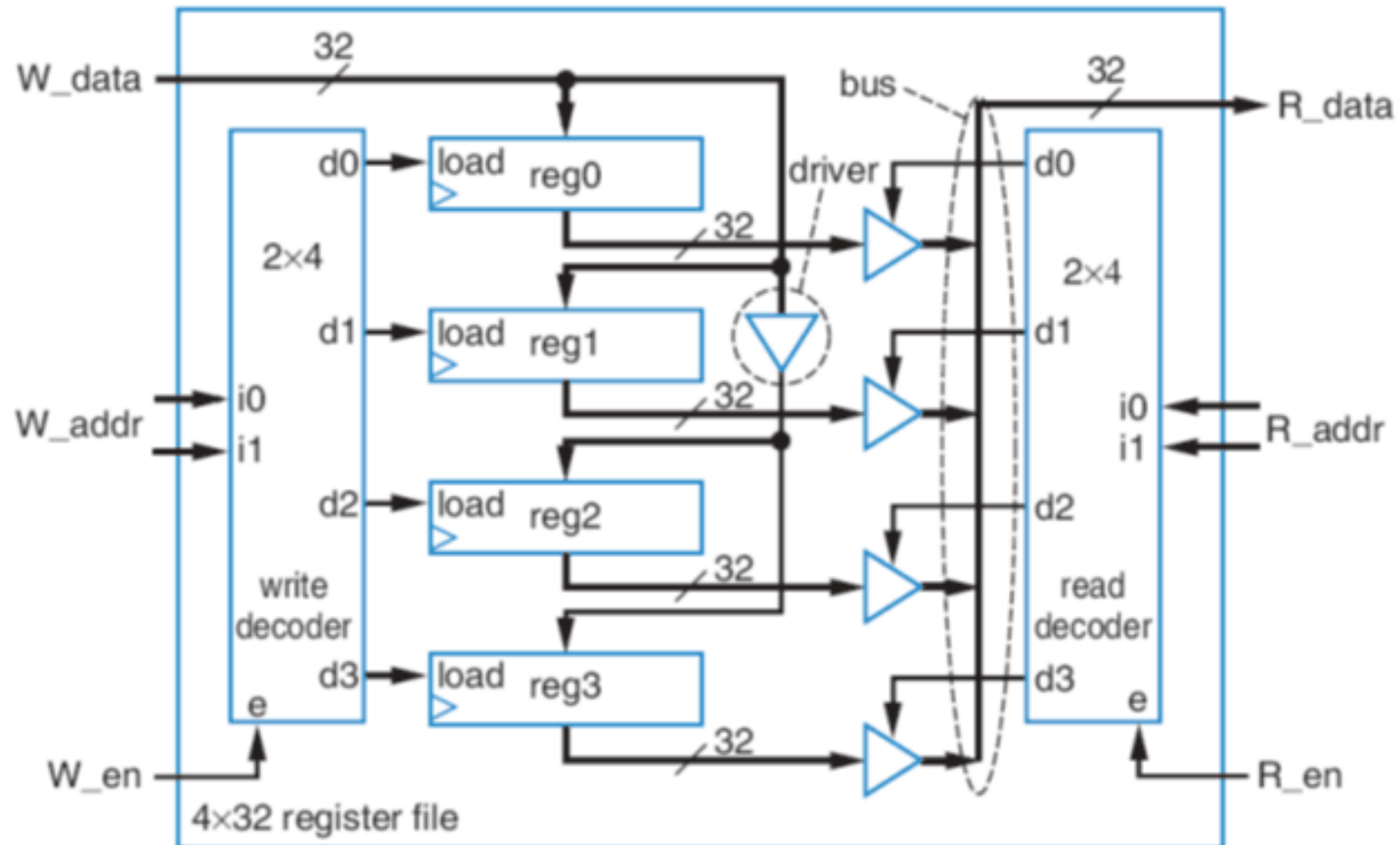

Shifters

General Description

  - Shifters are not Shift Registers: Shifters use MUX, and change value immediately
- $X \gg 1$ equals $X/2$
- $X \ll 1$ equals $X * 2$




Shifters

Bigger Shifter

- A shifter that can shift by any amount - By using multiple shifters
- To shift I by N, $4x+2y+z = N$, where $x, y, z = 0$ or 1 .

Q: $xyz=??? to$
shift I by 5?

 


Finite State Machine

General Description

- Finite State Machine (FSM) has states, inputs, outputs, initial state, transitions.
- State Diagram & State Table:

Inputs: b; Outputs: x

 

	Inputs			Outputs		
	s1	s0	b	x	n1	n0
<i>Off</i>	0	0	0	0	0	0
	0	0	1	0	0	1
<i>On1</i>	0	1	0	1	1	0
	0	1	1	1	1	0
<i>On2</i>	1	0	0	1	1	1
	1	0	1	1	1	1
<i>On3</i>	1	1	0	1	0	0
	1	1	1	1	0	0

Finite State Machine

FSM (Controller) Design

- Five steps:
 1. Capture the FSM
 2. Create the architecture
 3. Encode the states
 4. Create the state table
 5. Implement the combinational logic

Finite State Machine

FSM (Controller) Design

- One day, Engineering students are rushing to Long Bin Building from their dorms on Xuanhuai Avenue. They are busy reading about FSMs in their favorite textbook and aren't looking where they are going.
- At the same time, Math students are rushing the 5th Canteen to get their favorite Pan Fried dumplings on Longpo Road. They are solving differential equations in their minds and aren't looking where they are going either.
- Then, a serious injury occurs at the intersection of the two roads. A student, Bit, decides to solve this problem by using FSM.

Finite State Machine

FSM (Controller) Design

- Bit uses two traffic sensors, T_A and T_B , on Xuanhuai Ave. and Longpo Road, respectively.
 - Sensors show 0: students present
 - Sensors show 1: students not present
- Bit uses two traffic lights, L_A and L_B , to control traffic. The traffic lights has three mode.
(Green: 00, Yellow: 01, Red: 10)

Finite State Machine

FSM (Controller) Design

- The FSM controller updates on the rising edge of the clock signal:
 - At beginning, the lights are green on Xuanhuai Ave. and red on Longpo Road.
 - If traffic appears on Xuanhuai Ave., the lights do not change. When there is no longer traffic on Xuanhuai Ave., the light on Xuanhuai Ave. becomes yellow for a clock cycle before it turns red and Longpo road's light turns green.
 - Similarly, the Longpo road's light remains green as long as traffic is present, then turns yellow and eventually red.

Finite State Machine


FSM (Controller) Design

- Step 1: Capture the FSM
 - Among all transitions leaving a state, only one condition should be true.
 - Among all transitions leaving a state, one condition must be true.
 - All conditions must be considered when leaving a state.

Finite State Machine

FSM (Controller) Design

- Step 2: Create the architecture

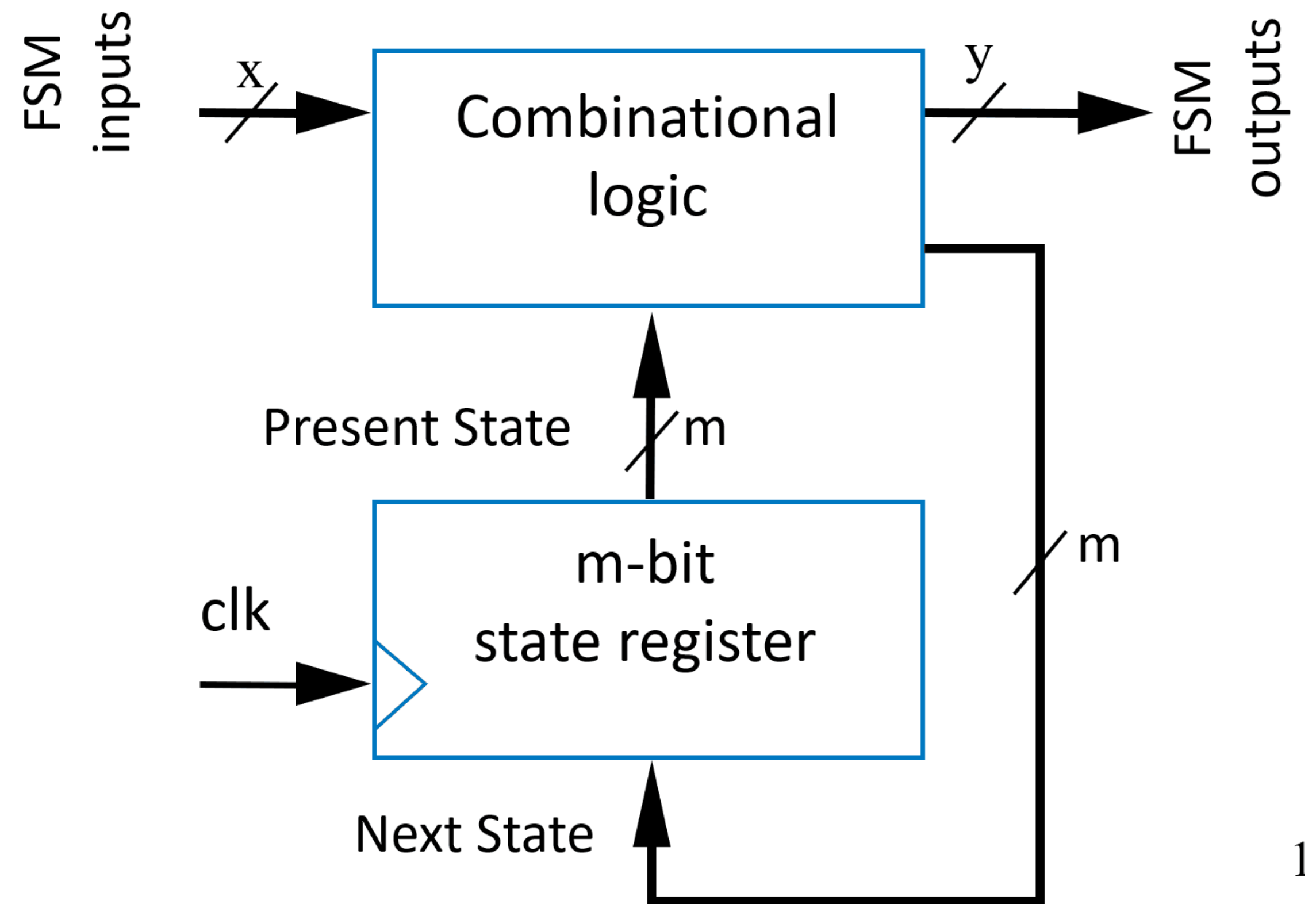

Finite State Machine

FSM (Controller) Design

- Step 3: Encode the states

Finite State Machine

FSM (Controller) Design

- Step 4: Create the state table

Finite State Machine

FSM (Controller) Design

- Step 5: Implement the combinational logic

Any Questions?